


Research Status of the National Key Laboratory of Power Electronics



Prof. Dr. Mark Dehong XU
College of Electrical Engineering
Zhejiang University
China
Email: xdh@cee.zju.edu.cn

Location of Zhejiang University

China

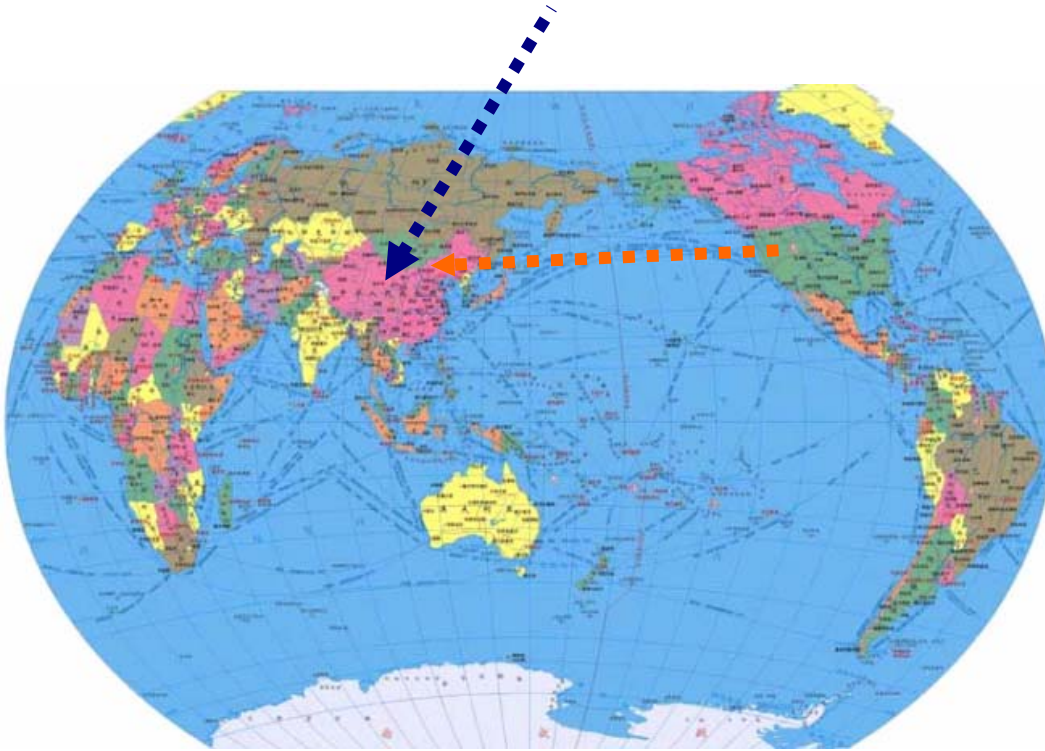

Zhejiang is Province name
Located in **Hangzhou** city: beautiful city in China
200km from Shanghai



Zhejiang University

Found in 1897

Key national university, Ranks the 3rd in China

The most comprehensive university in China

Agriculture and
Biotechnology

Animal Sciences

Biomedical Engineering and Instrument Science

Computer Science (Software Technology)

Civil Engineering and Architecture

Economics

Education

Electrical Engineering

Environmental and Resource Sciences

School of International Studies

Humanities

Information Science and Engineering

Law

Life Sciences

Mechanical and Energy Engineering

Materials Science and Chemical Engineering

Medicine

Management

Pharmaceutical Sciences

Science

Public Administration

Statistics of 2004

Undergraduates: 24983

Master students :11883

Doctor students:6050

Oversee student:1235

Research Funds 1.02 billion yuan

Papers Included in SCI (2004) 1917


Papers Included in EI (2004) 1551

Granted Patents (2004) 330



The college of Electrical Engineering

Established in 1920

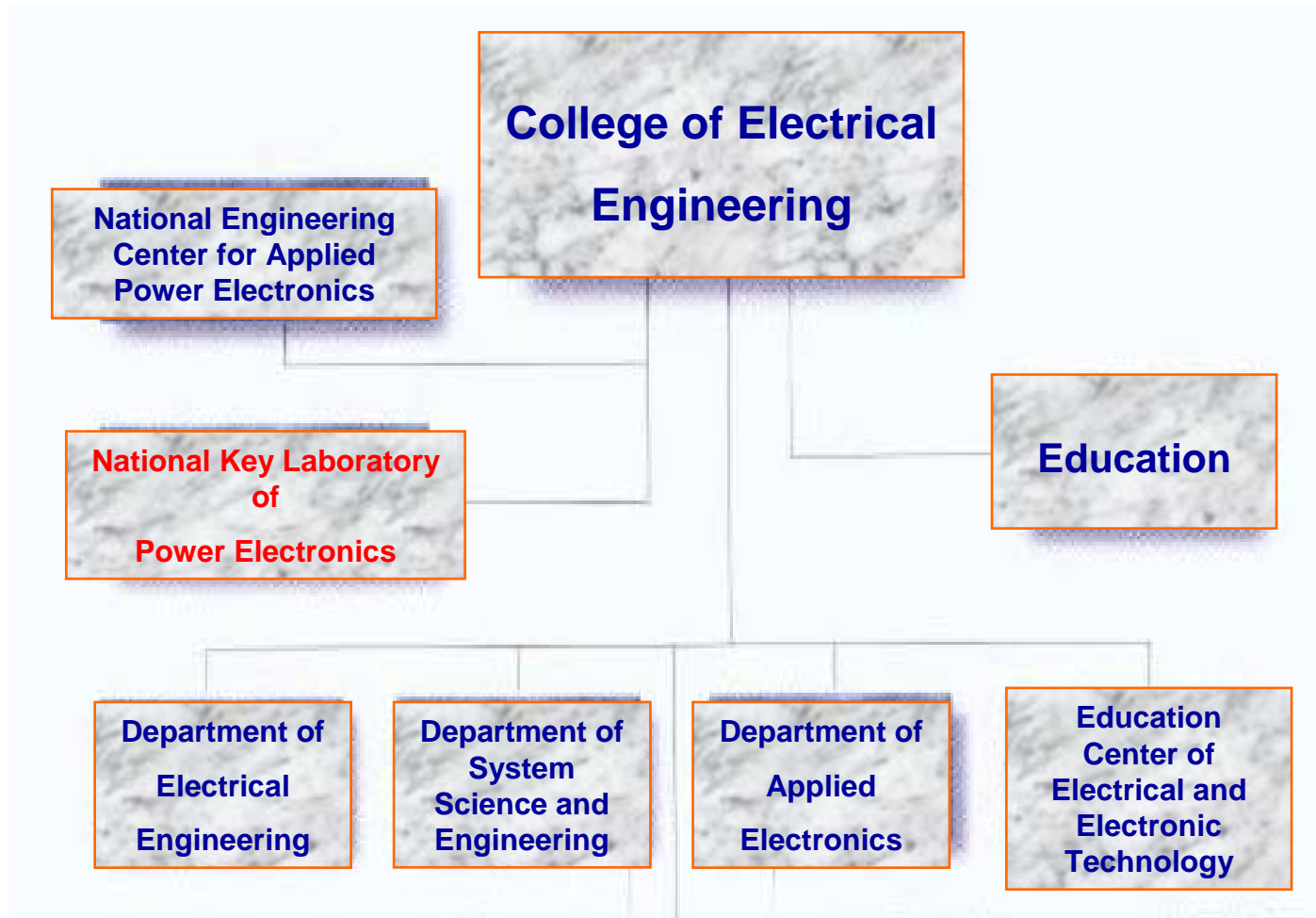

Brief information

- The first SCR media-frequency induction-heating power supply (100kW/1kHz) in 1971 in China,
- 1981 began recruit graduates for postgraduates
- 1988, 2002, National key discipline
- 1989 become National Key Laboratory of Power Electronics

Staff:

One member of China Academics of Engineering

Professors:8

Associate professors:4

Assistant professors:7

Students:

Master students: accept 50/year

Ph. D students: accept 25/year

Lab facilities

Software:

Saber, Ansoft(SIMPLORER, Maxwell, PExprt, RMxprt), Matlab, Mathcad, dspace

Instrument:

Network analyzer, device test equipments, power analyzer, logic analyzer ,EMC test equipments, so on

Package equipments:

QualMark FALT &HASS System, SMT equipments




Research directions

- Soft switching technology
- Inverter and UPS control
- Power Electronics for Power system
- Renewable power generation system
- Inverters for induction heating and HV processing equip.
- Integrated power electronics
- Drive
- EMI/EMC

Boost power factor correction (PFC) converter

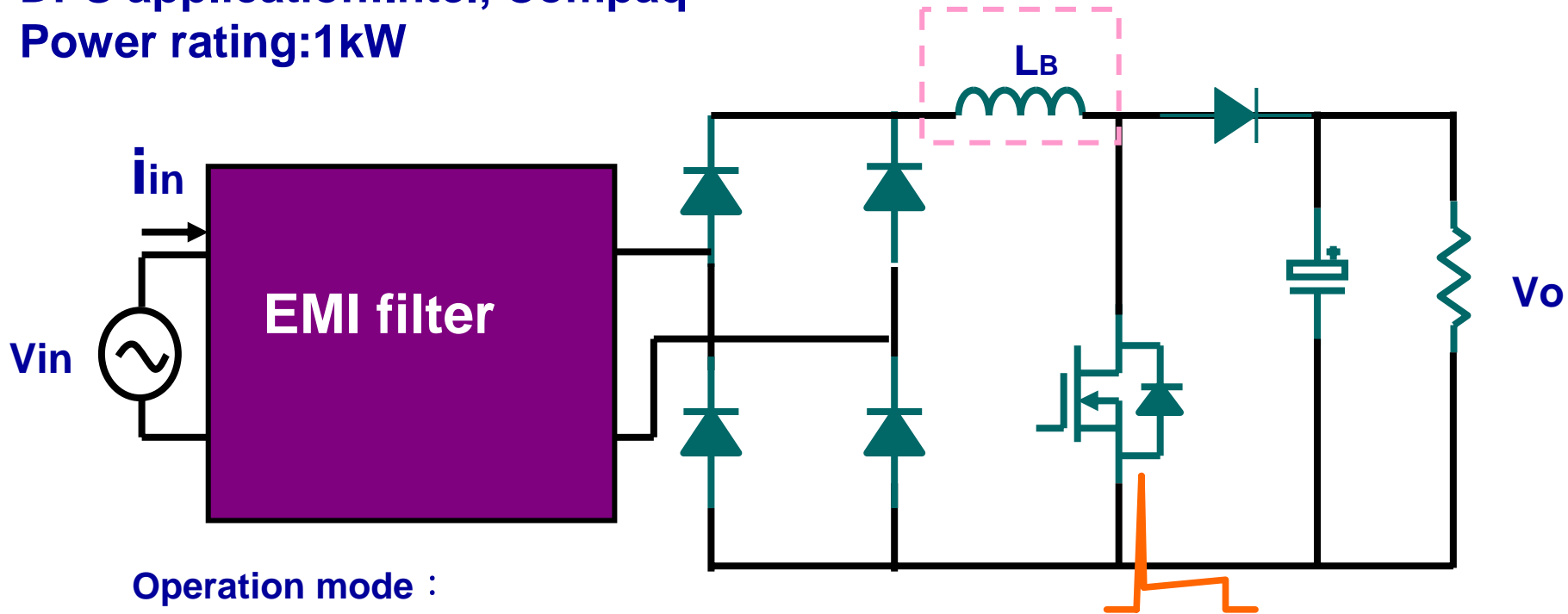DPS application: Intel, Compaq
Power rating: 1kW



Operation mode :


Current continuous mode (CCM) is preferred instead to DCM

- lower current stress, lower conducting loss
- small magnetic component size and its loss ($L_B + EMI$)
- Higher reverse recovery loss

Diode reverse recovery resulting loss suppression


- Lossless snubber
- ZCS or ZVS quasi resonance (DCM)
- ZVT switching
- Active clamping
- SiC diode

Active clamping

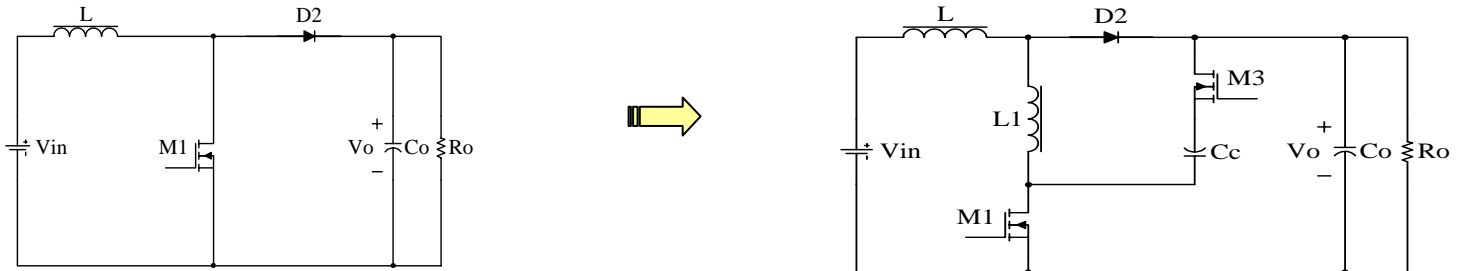


Both the main switch and auxiliary switch are ZVS

Parasitic resonance in active clamping

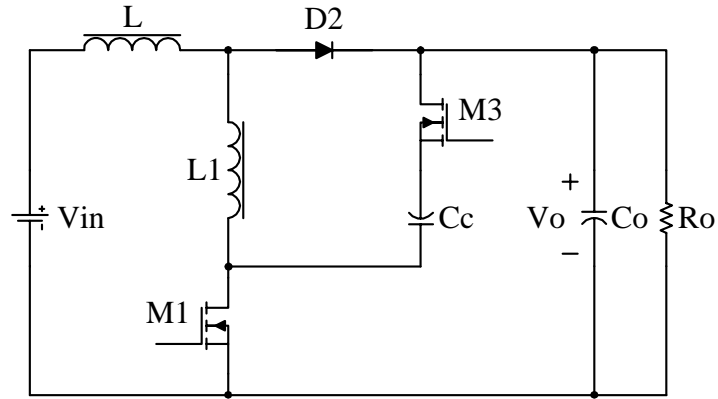

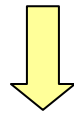$M1$ in on-state, resonance between $L1$ and $D2$




$D2$ voltage stress = $2 V_o$



$M1$ and $M3$ gate signal are complimentary



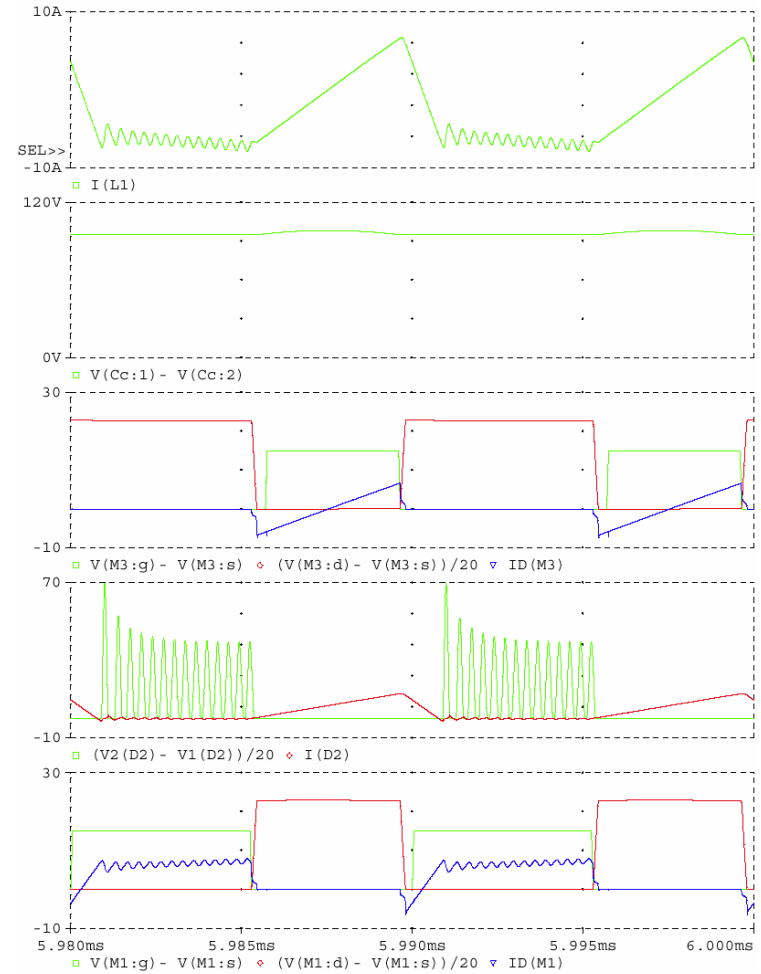Terminal voltage of $D2$ in off-state is not clamped




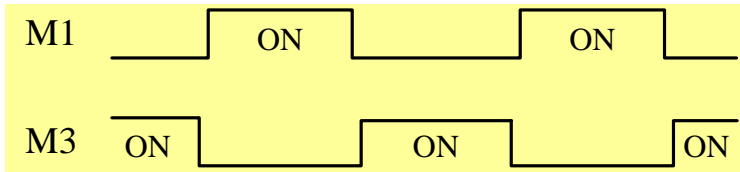
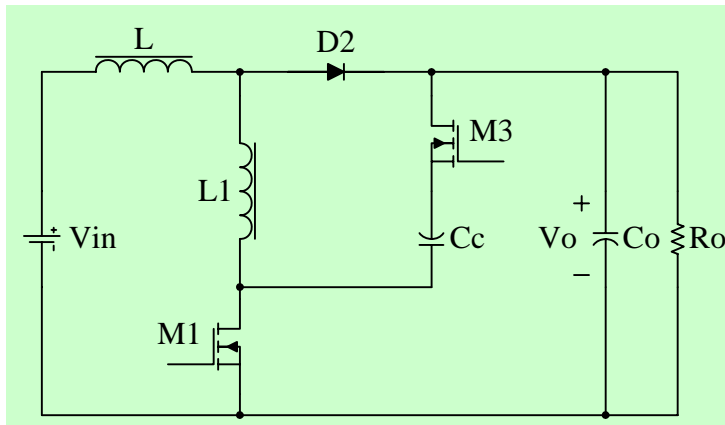
Compound-Active-Clamping (CAC) Boost Converter



Conventional active-clamping boost converter

(M1, M3) in complimentary mode

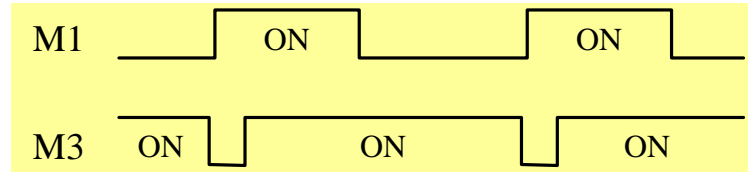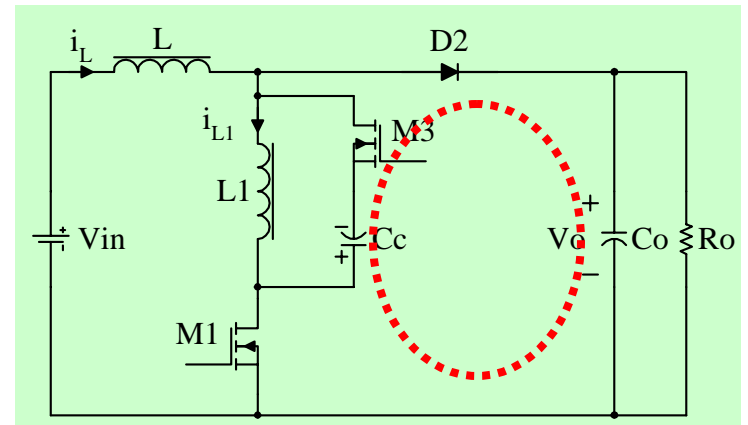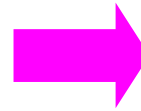- **Key piont:** $V_{s1} + V_{s3} + V_{d2} = V_o + V_{Cc}$
- Only 2 of 3 device are conducting
- Terminal voltage of the turn-off device is clamped and parasitic oscillation is eliminated
- Suppress reverse recovery process
- Both main and aux. switch are ZVS



Compound-Active-Clamping (CAC) boost converter



2 of the 3 devices in conducting

(M1, M3 and D2)


Soft switching DC/DC converter and PFC converter

Compound-Active-Clamping (CAC) ZVS PFC

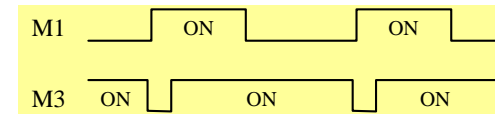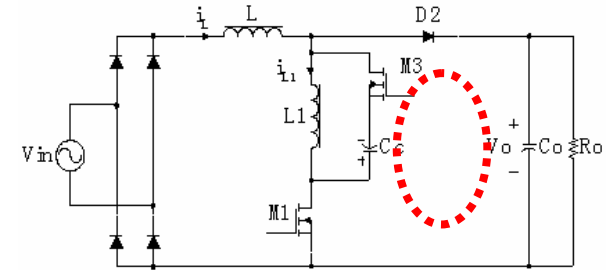- Diode reverse recovery is relieved. No voltage ringing occurs on the diode.
- Both the main switch and the auxiliary switch are ZVS.
- Higher efficiency is achieved for 1kW CAC PFC converter



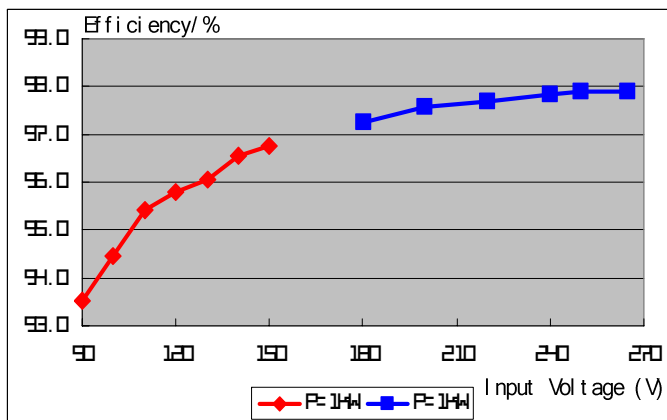The main switch and the auxiliary switch do not operate in complimentary mode. **There are always two of the three devices (M1, M3 and D2) in conducting, which results in clamping the terminal voltage of the turn-off device.**



Efficiency vs. input voltage V_{in}
($P_o=1000W$, $V_o=380Vdc$)

Input voltage $V_{in}=90V\sim 265Vac$
Output voltage $V_o=380Vdc$
Rated power $P_o=1kW$
Switching frequency $f_s=100kHz$


- S1 and S3: IRFP460×2
- D2: MUR1560
- C2: 4000pF/1kV
- Cc: 2.2uF/250V
- L1: 8uH
- L: 600uH




Minimum-Voltage Active-Clamping(MVAC) PFC Converter

- Diode reverse recovery relieved.
- No voltage ringing on the diode.
- Both the main switch and the auxiliary switch are ZVS.
- Higher efficiency
- Voltage stress equal to hard-switching circuit

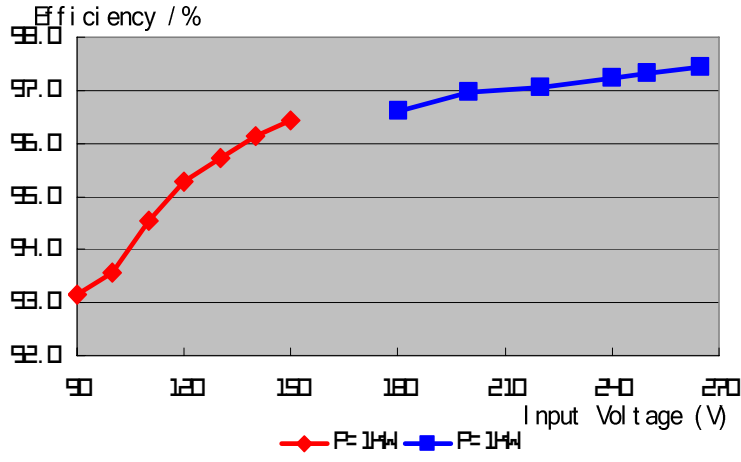PWM control is the same as CAC ZVS PFC converter




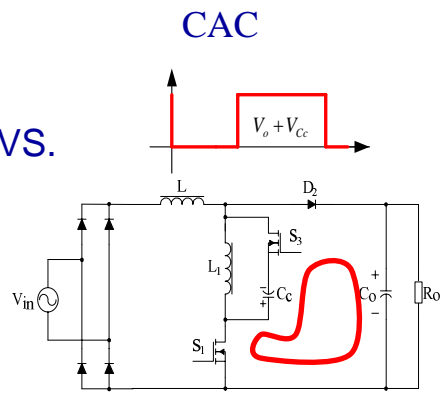Efficiency vs. input voltage V_{in}
($P_o=1000W, V_o=380Vdc$)



$$V_{s1} + V_{s3} + V_{d2} = V_o + V_{Cc}$$


Minimum Voltage Active Clamp

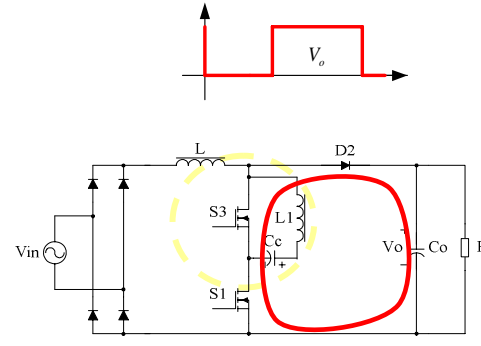

$$V_{s1} + V_{s3} + V_{d2} = V_o$$



Input voltage $V_{in}=90V\sim 265Vac$
 Output voltage $V_o=380Vdc$
 Rated power $P_o=1kW$
 Switching frequency $f_s=100kHz$

- $S1, S3$: IRFP460×2(IR)
- $D2$: MUR1560
- L : 0.6mH (EE55)
- $C2$:1680pF/1000V
- C_o : 1320µF/450V
- $L1$: 12µH
- Cc : 4.7µF/250V

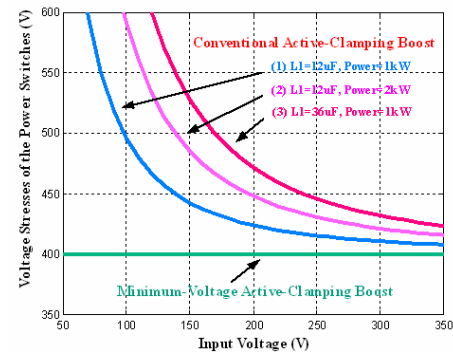

CAC 3-phase PFC converter

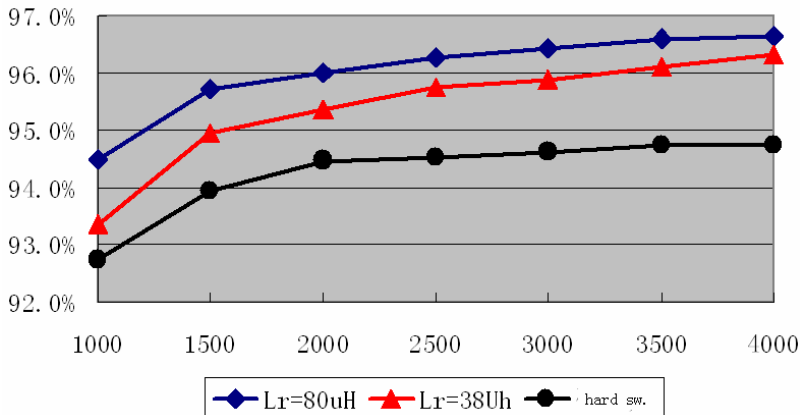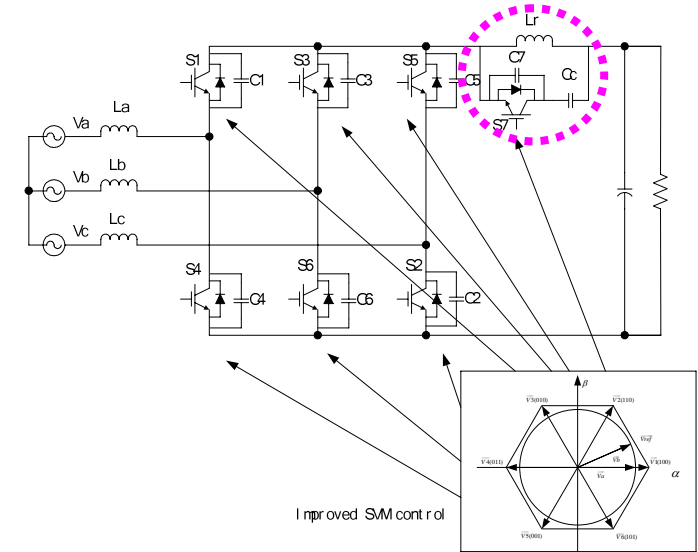- Add one auxiliary branch
- ZVS for all the switches
- Improved SVM control
- Suppress diode reverse recovery
- Fixed frequency control for both the main switch and the auxiliary switch
- low voltage stress on the switches
- Higher efficiency
- Lower EMI






Vin: 3*380Vrms Vdc=620V Pout=4kW
switching freq. 12.8kHz


Sector	angle	Vector1	Zero vector	Vector2	Vector1
1	$-30^\circ \sim 0^\circ$	1 0 0	1 1 1	1 0 1	1 0 0
2	$0^\circ \sim 30^\circ$	1 0 0	1 1 1	1 1 0	1 0 0
3	$30^\circ \sim 60^\circ$	1 1 0	0 0 0	1 0 0	1 1 0
4	$60^\circ \sim 90^\circ$	1 1 0	0 0 0	0 1 0	1 1 0
5	$90^\circ \sim 120^\circ$	0 1 0	1 1 1	1 1 0	0 1 0
6	$120^\circ \sim 150^\circ$	0 1 0	1 1 1	0 1 1	0 1 0
7	$150^\circ \sim 180^\circ$	0 1 1	0 0 0	0 1 0	0 1 1
8	$180^\circ \sim 210^\circ$	0 1 1	0 0 0	0 0 1	0 1 1
9	$210^\circ \sim 240^\circ$	0 0 1	1 1 1	0 1 1	0 0 1
10	$240^\circ \sim 270^\circ$	0 0 1	1 1 1	1 0 1	0 0 1
11	$270^\circ \sim 300^\circ$	1 0 1	0 0 0	0 0 1	1 0 1
12	$300^\circ \sim 330^\circ$	1 0 1	0 0 0	1 0 0	1 0 1

Hard switching
 ZVS
 ZVS

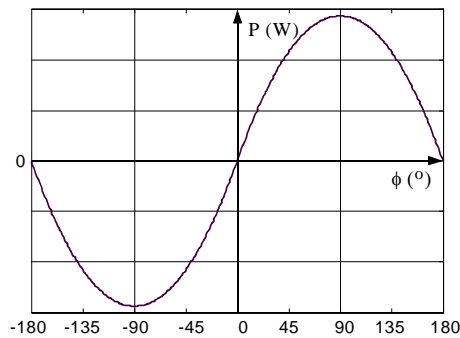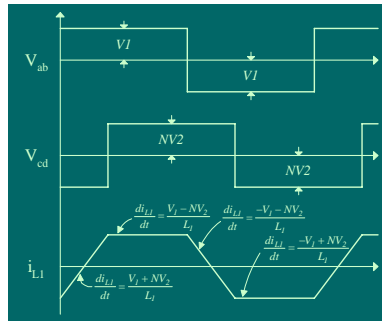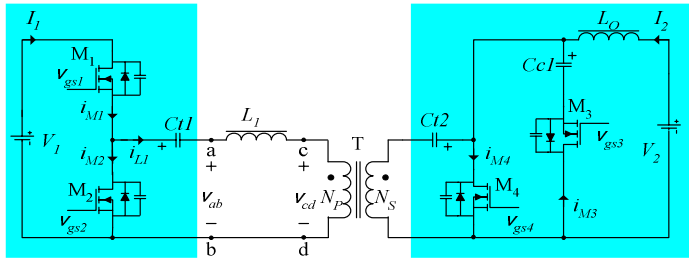
Phase shift (PS) controlled bidirectional DC/DC converter



Power vs. phase-shift

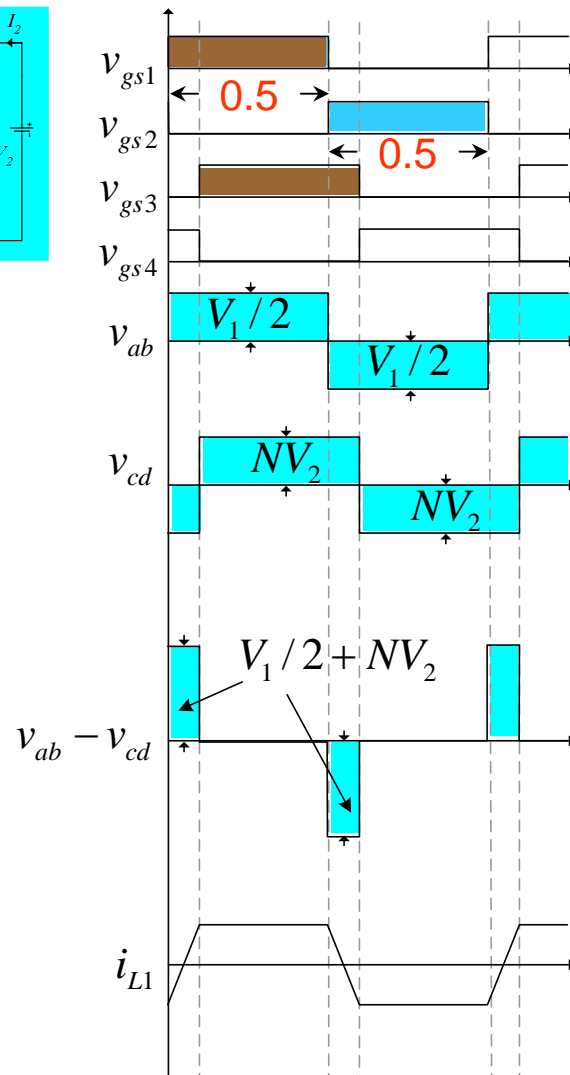

PS control when $V_1/2 = NV_2$

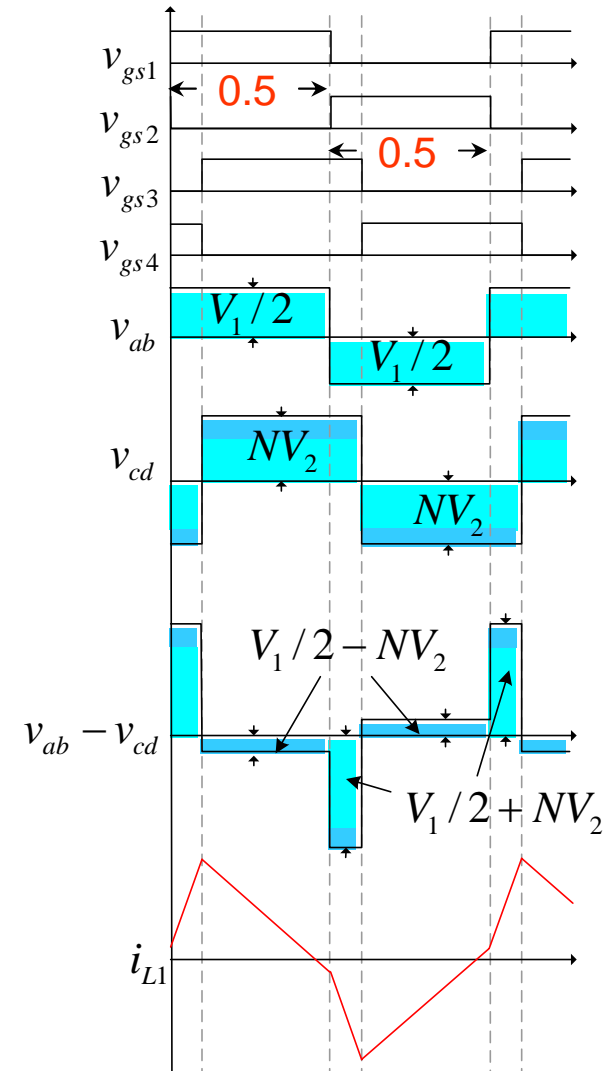

PS control when $V_1/2 < NV_2$



PWM+phase shift (PPS) control

PPS control, duty ratio of M1 AND M3:


N : turn ratio of the transformer

Duty ratio of M2 and M4 : $1-D$


$$D = \frac{NV_2}{V_1}$$

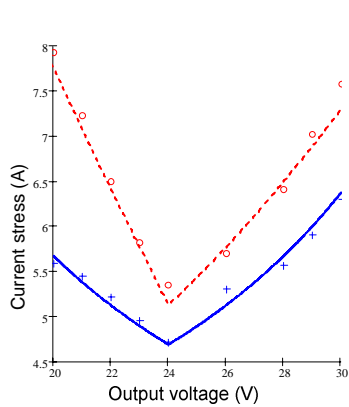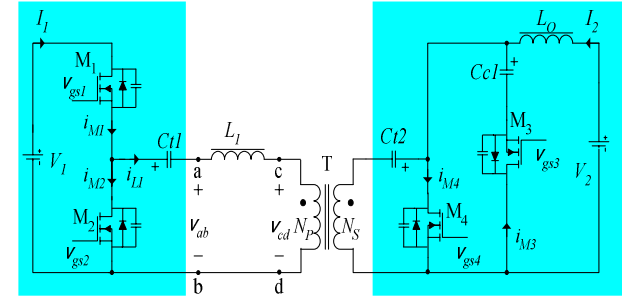

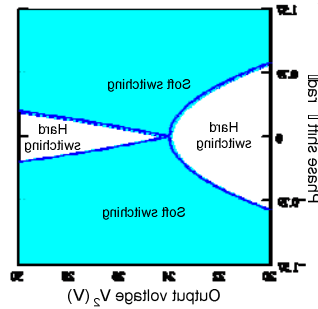
○ Pspice simulation points under PS control
--- Calculation results under PS control
+++ Pspice simulation points under PPS control
--- Calculation results under PPS control




PS control

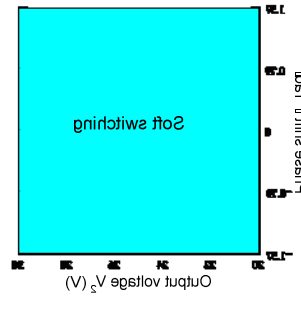

PPS control



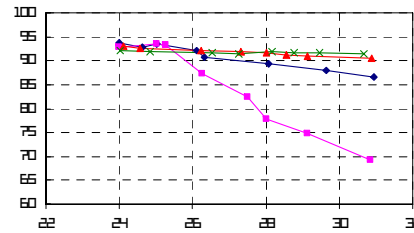


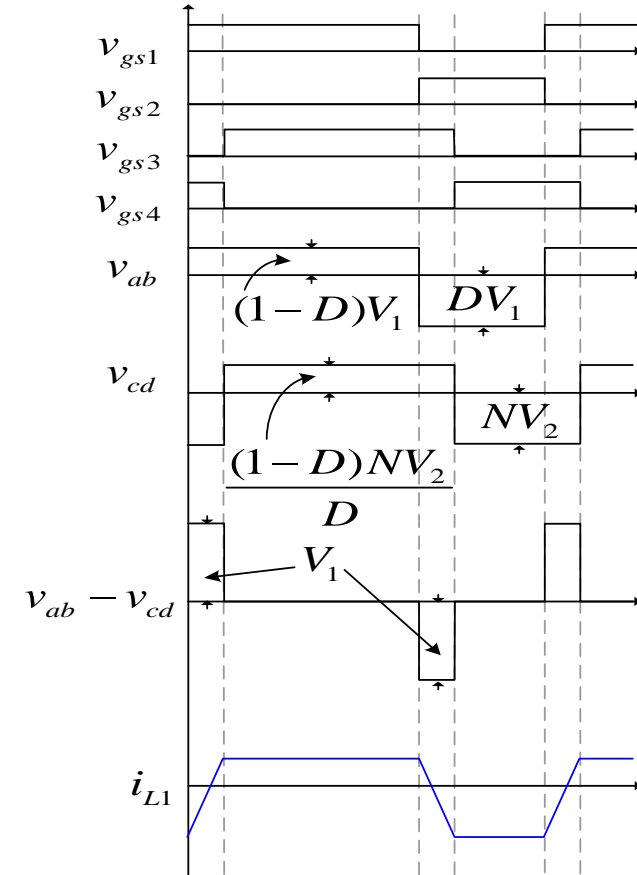◆ The efficiency curve under PS control (100W-output)
■ The efficiency curve under PS control (30W-output)
▲ The efficiency curve under PPS control (100W-output)
× The efficiency curve under PPS control (30W-output)










- Current peak is reduced
- switching loss and conduction loss reduced
- Current stress of the switches are reduced
- ZVS range is wider

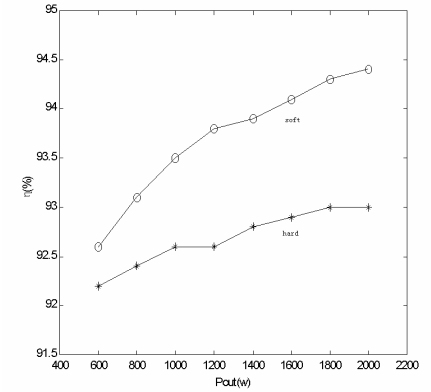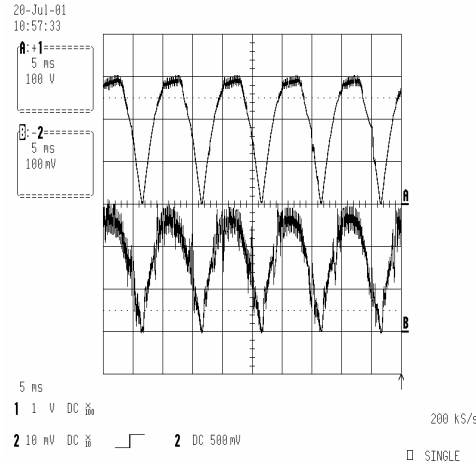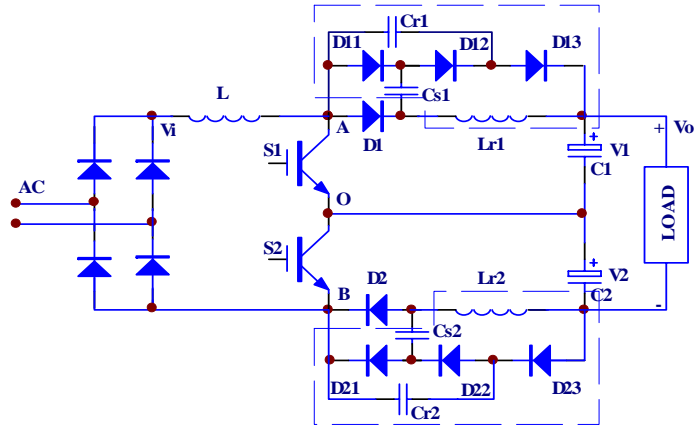Three-level Power Factor Correction with Passive Lossless Snubber



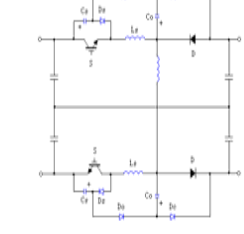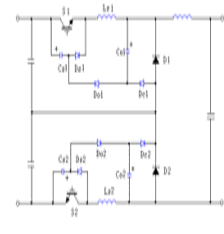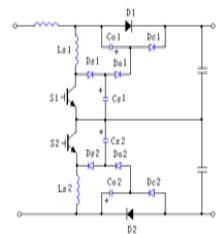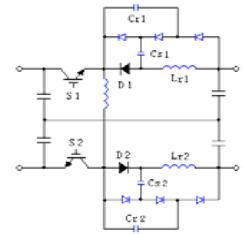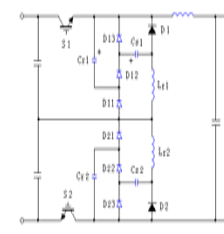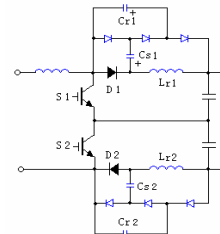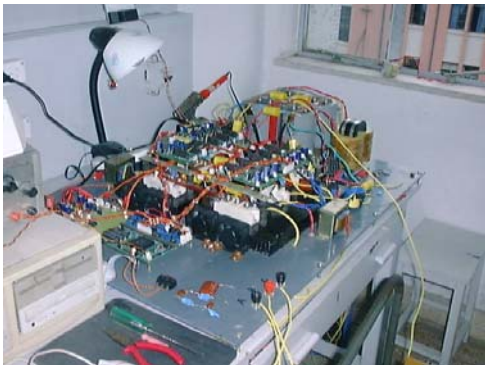- efficiency is increased
- Less over-voltage stress on main power switches.



Chargers



- Input voltage $220\text{Vac} \pm 15\%$
- Output voltage $180\text{V}-275\text{V}$, output current 15A
- PFC operate frequency 33KHz , DC/DC operate frequency 70KHz
- One module output power 4kW , efficiency $>90\%$



- Three phase input voltage $380\text{Vac} \pm 20\%$
- Output voltage $175\text{V}-330\text{V}$, output current 25A
- PF : 0.92 , Efficiency : 90%


Power supply

100VA DC/DC Converter



2-Phase 25Hz/3kVA AC Source
(Parallel and Play and Plug in Available)

500VA DC/DC Converter

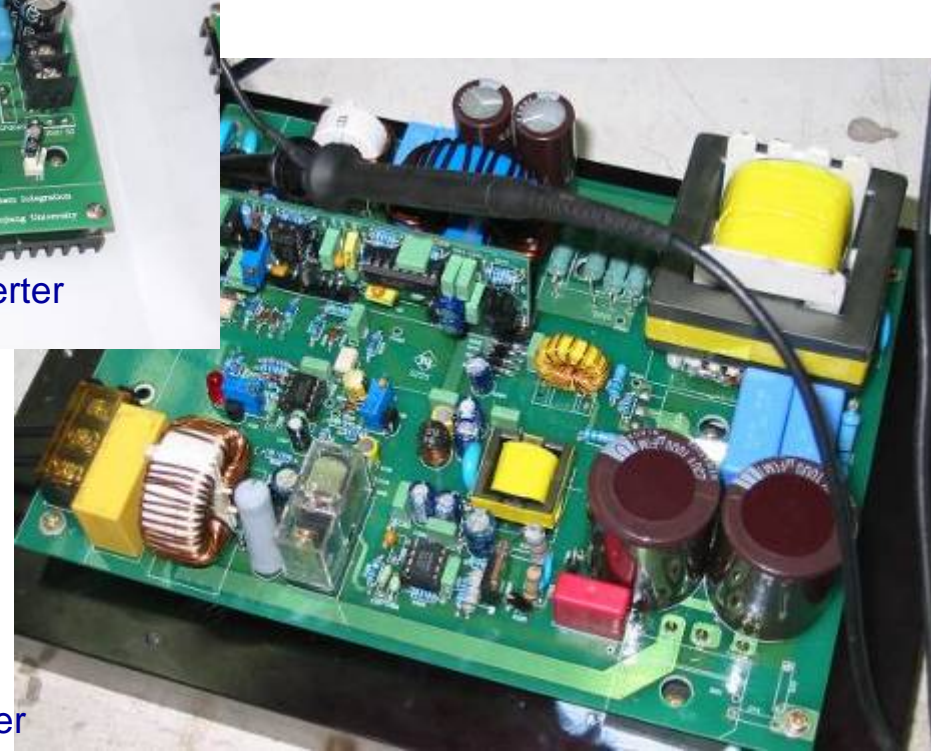


3kVA/50Hz AC/DC/AC Inverter


Integrated power electronics

- Planar transformer design
- Integrating passives design
- packaging
- Power management IC design


PFC controller

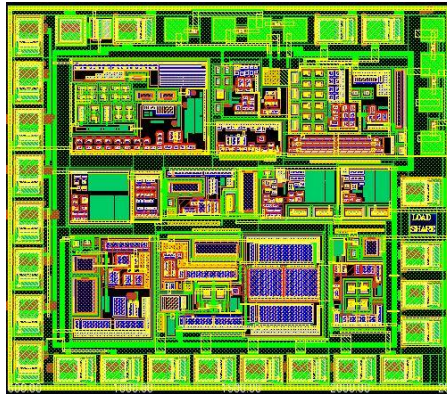


0.9V/50A VRM

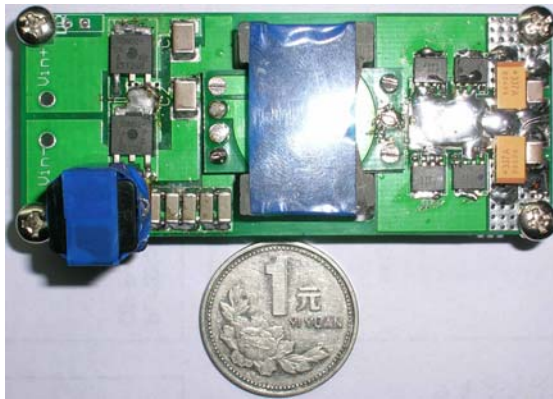

Current sharing

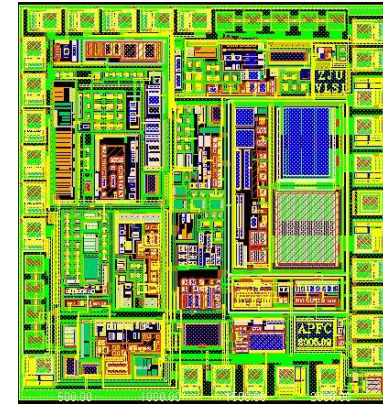


DC/DC Module: 1/4 Brick, 480VA, 48/9V

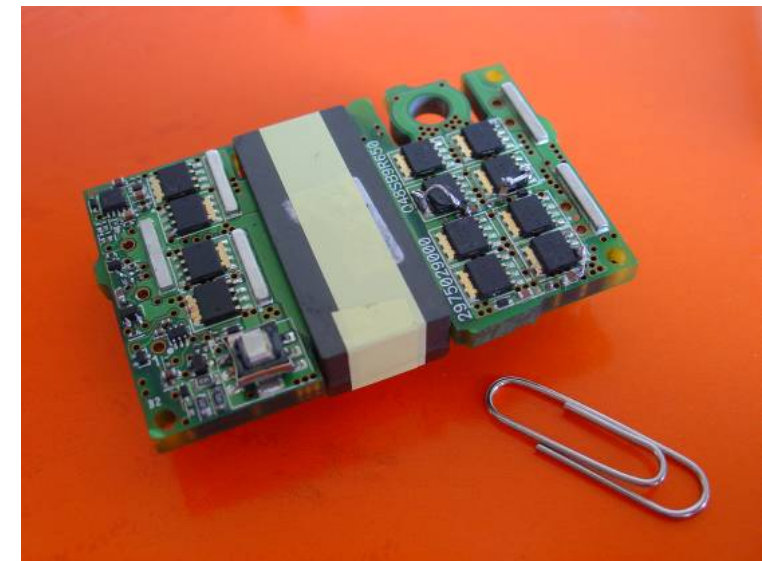


30kW UPS with DSP control

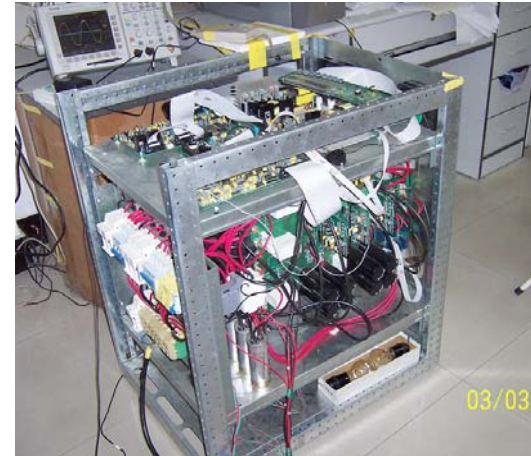
- DSP control
- 3in-3out without transformer
- Front end PFC
- Current sharing for multi-UPS



Light load to heavy load

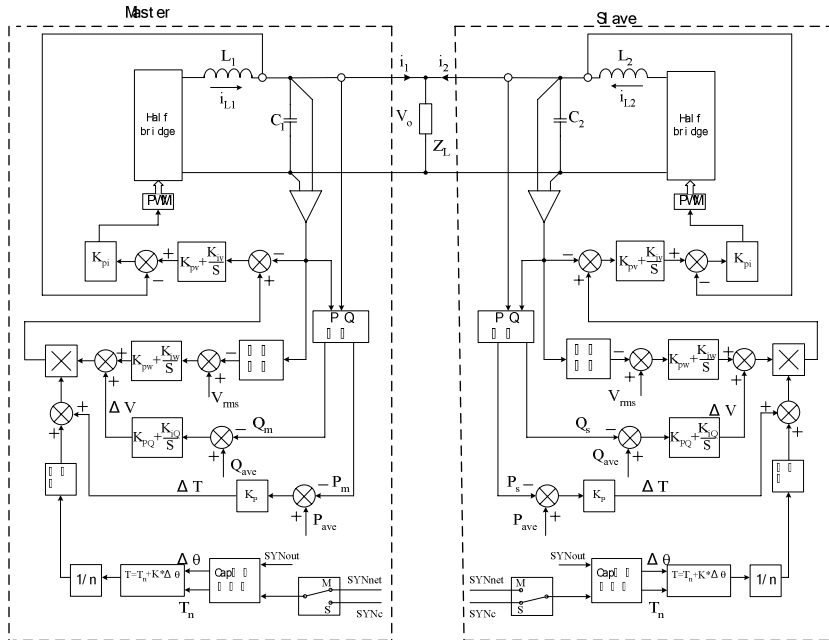

Current sharing control




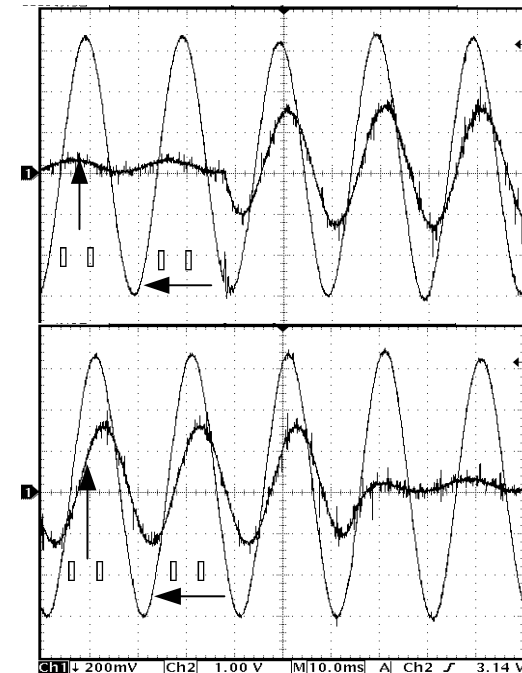


Heavy to light

V:100V/div, Current:11A/div, time:10mS/div

Novel PWM Method for Flying Capacitor Multilevel Inverters

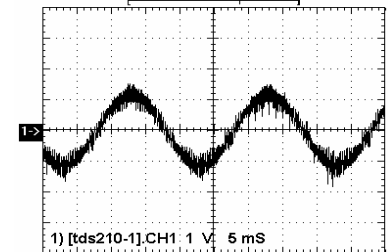
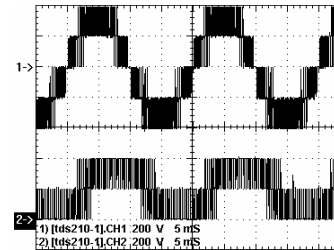
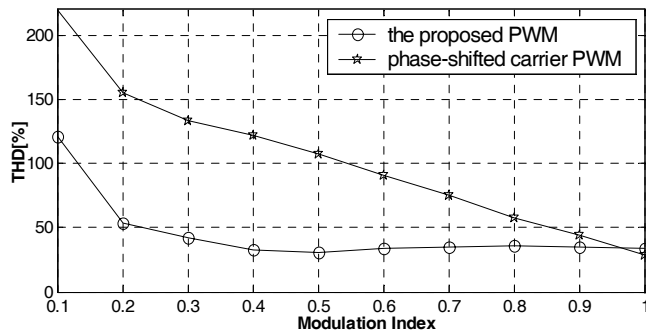
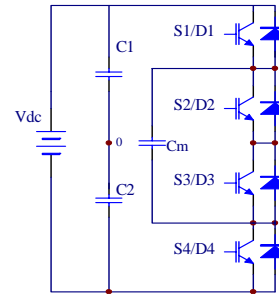
- good performances under both high and low modulation index regions.
- balances the flying capacitor voltage in a carrier period.



THD vs. modulation index (below 150th harmonics)

Phase- and line- voltages


Current waveform

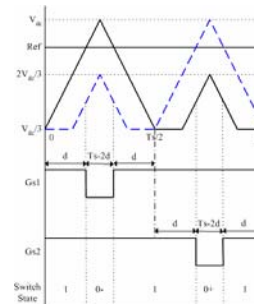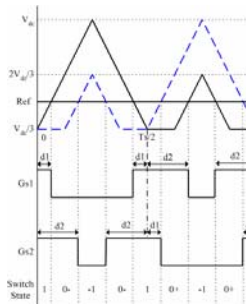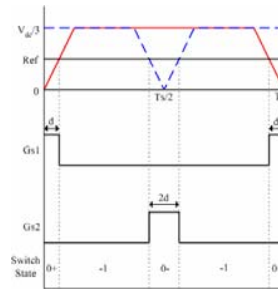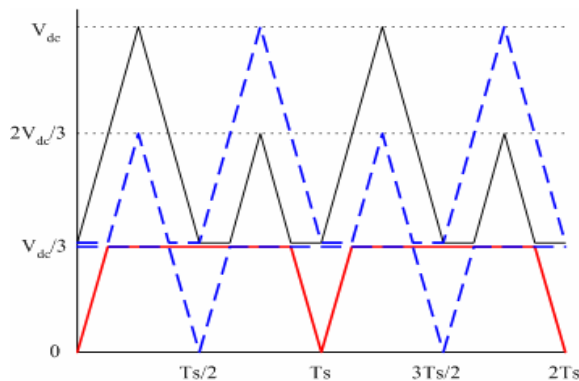


35kJ/7.5kW/200A HTS SMES

- Current unbalancing in a multi-modular current source converter with Carrier-swapping
- Lower AC side harmonics current
- The response of the converter is fast.



Test setup

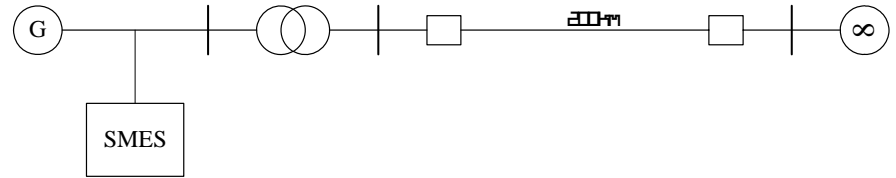

Without SMES

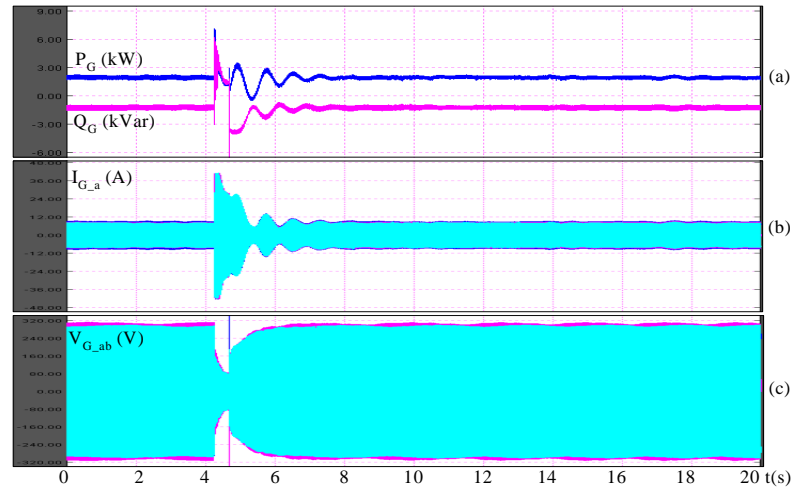

With SMES

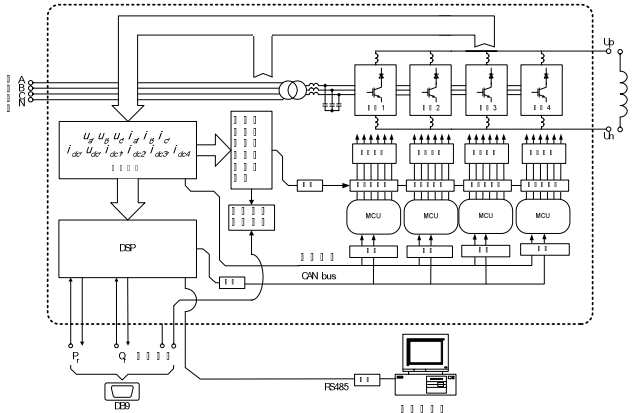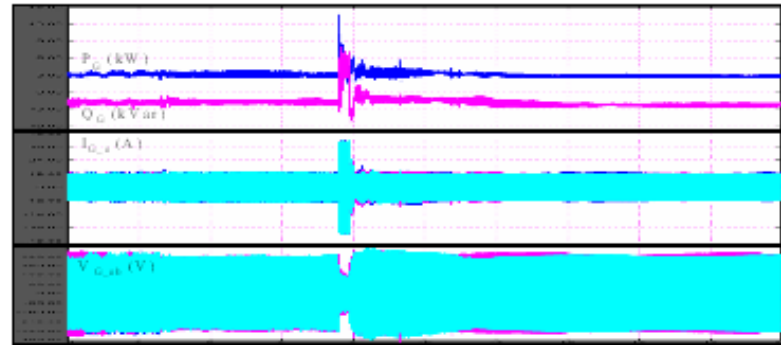

Power System Failure Current Limiter (10kV / 1000A)



Transformer



*Semiconductor
Limiter*



Sensors






Isolated Trigger

Active Power Filter




Vin:380Vrms Rating : 15KVA

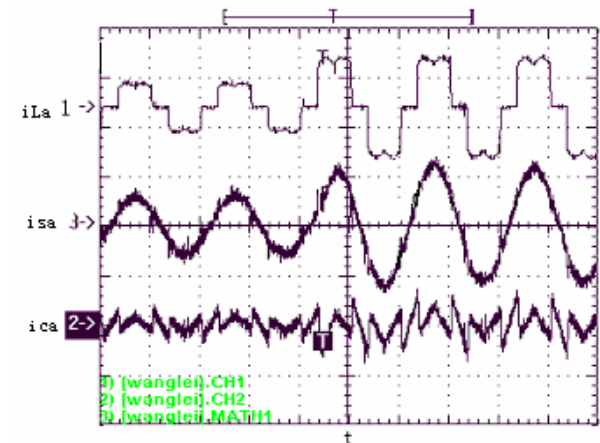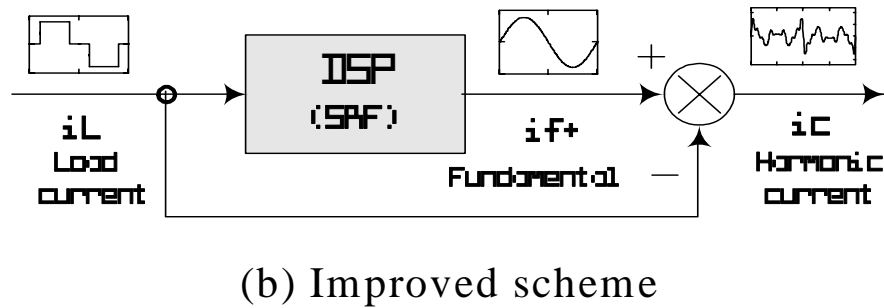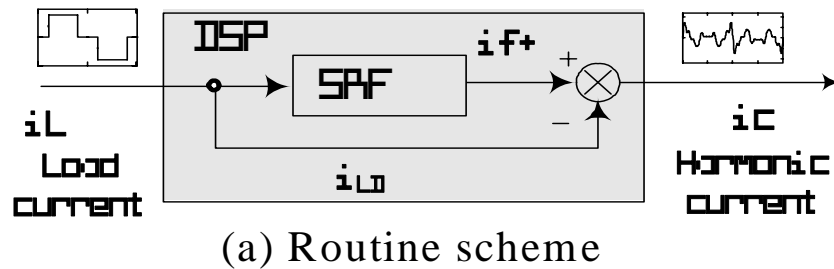- DSP control
- Accurate compensation method with digit control
- Higher efficiency conversion Tech.
- Inductorless bus bar





Dynamic response (32A/div, 10ms/div)

50 kVA active power quality conditioner

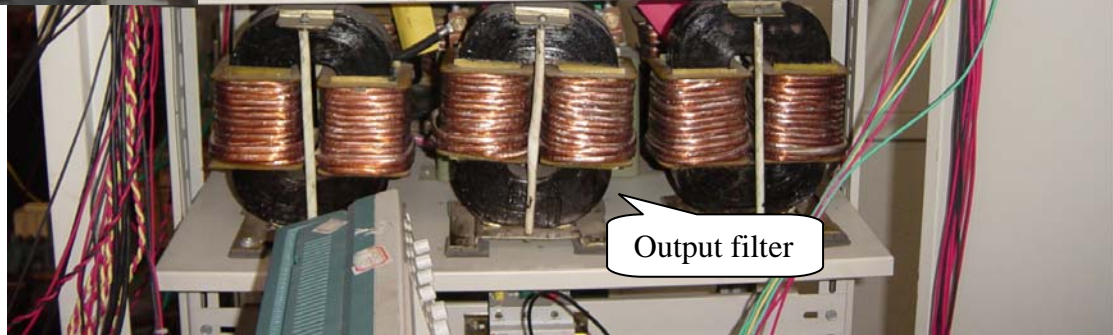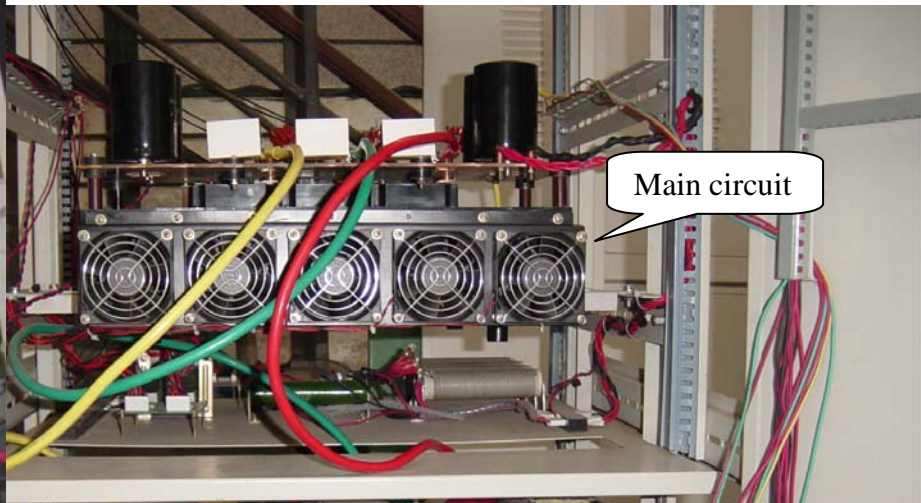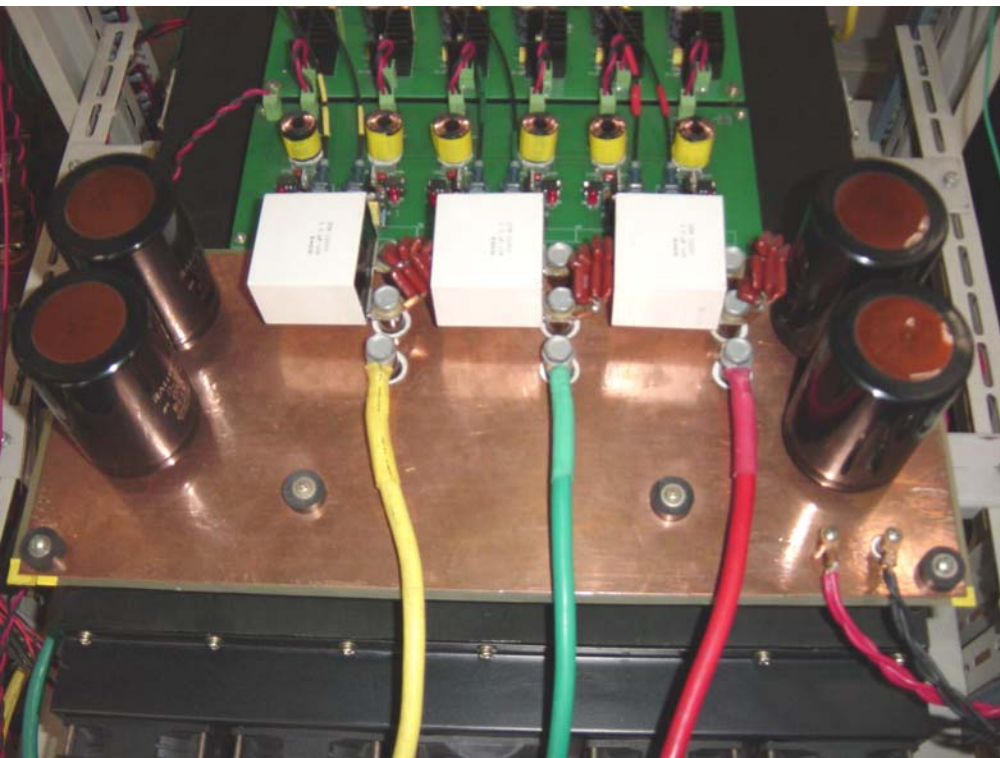




5 kW Fuel cell power generation system

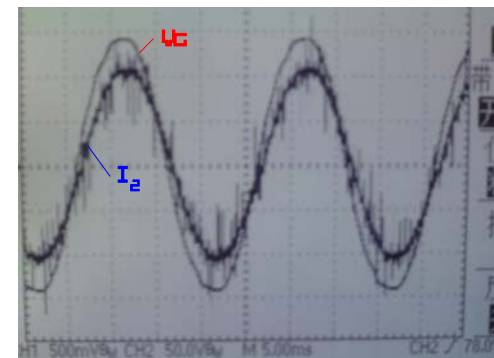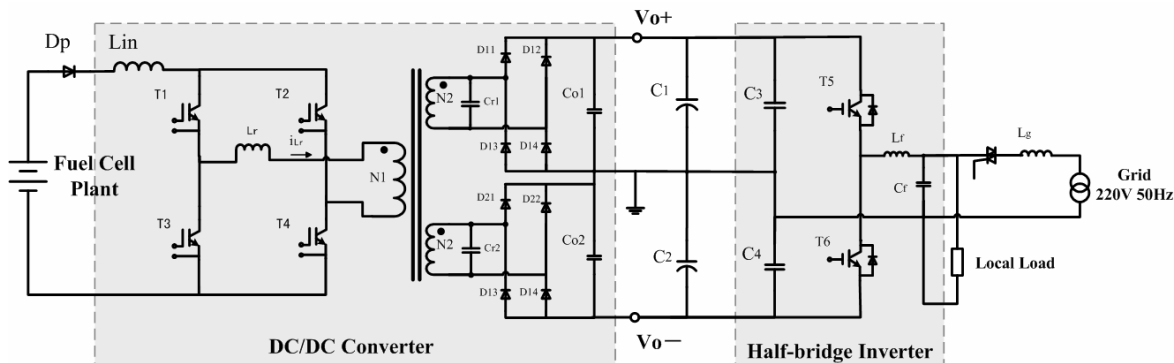- Front end current ZCS DC/DC with RB-IGBT suited to FC
- Seamless transition by amplitude adjusting
- LCL filter fed inverter stability improvement by split capacitor mid-point current feedback



$V_c: 100V/div$

$I_c: 6.4A/div$

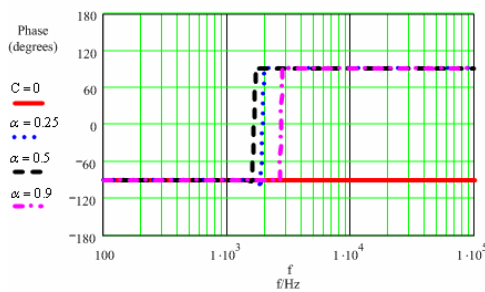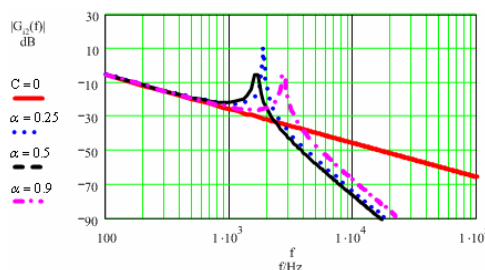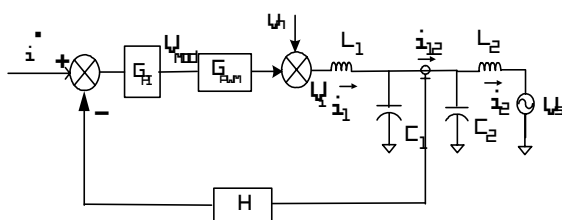

Inverter for inducting heating



200kW/50kHz IGBT
inverter for induction heating



5-30kW/100-400KHz MOSFET
inverter for induction heating



Heating process line




High Voltage Ion Generator for plastic film Printing



Motor Drive

Drive equipment for spaceship

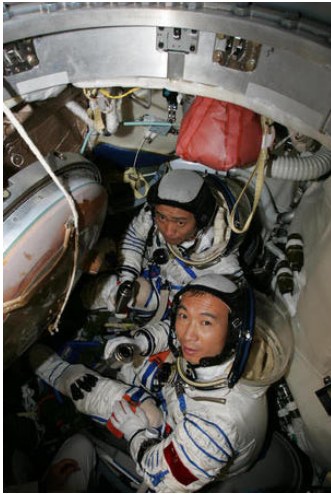

PM brushless DC motor for lockstitch sewing machine




1kVA Matrix Converter



20kVA PM Brushless Inverter



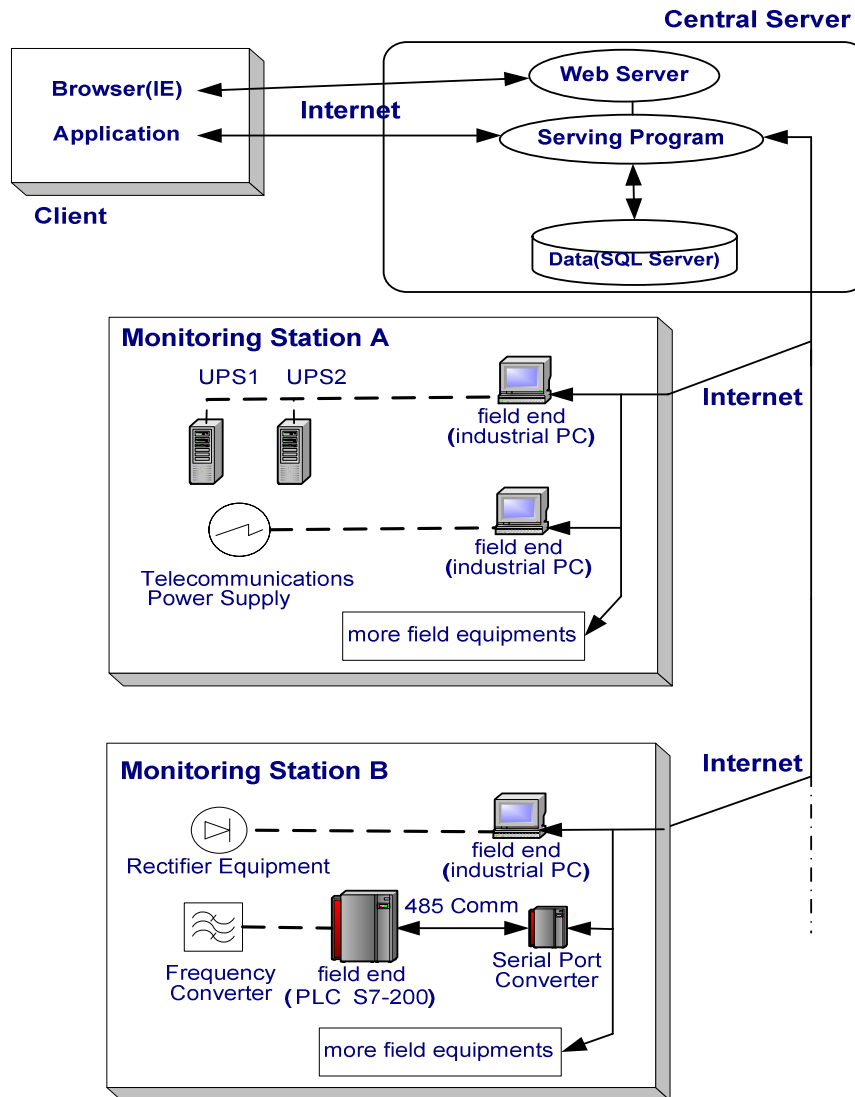Remote fault diagnosis for power electronics equipment



- Compatibility design of remote fault diagnosis system for different power electronic equipments
- Remote real-time and synchronous data acquisition and transfers method
- On-line and off-line fault diagnosis for power electronic systems

Training Tool:

Digital Control Platform for Power Electronics



Future research focus

Fundamental oriented

- Power electronics Integration technology
- High frequency conversion
- Advanced control in power electronics
- Virtual testing for power electronics
- Thermal design
- EMI filter design

Application oriented

- Power Electronics for renewable and cleaning power generation
- EV and power electronics for transportation
- Power Electronics application in environment protection and materials' treatment
- FACT devices
- High voltage, large power drives

Thanks!