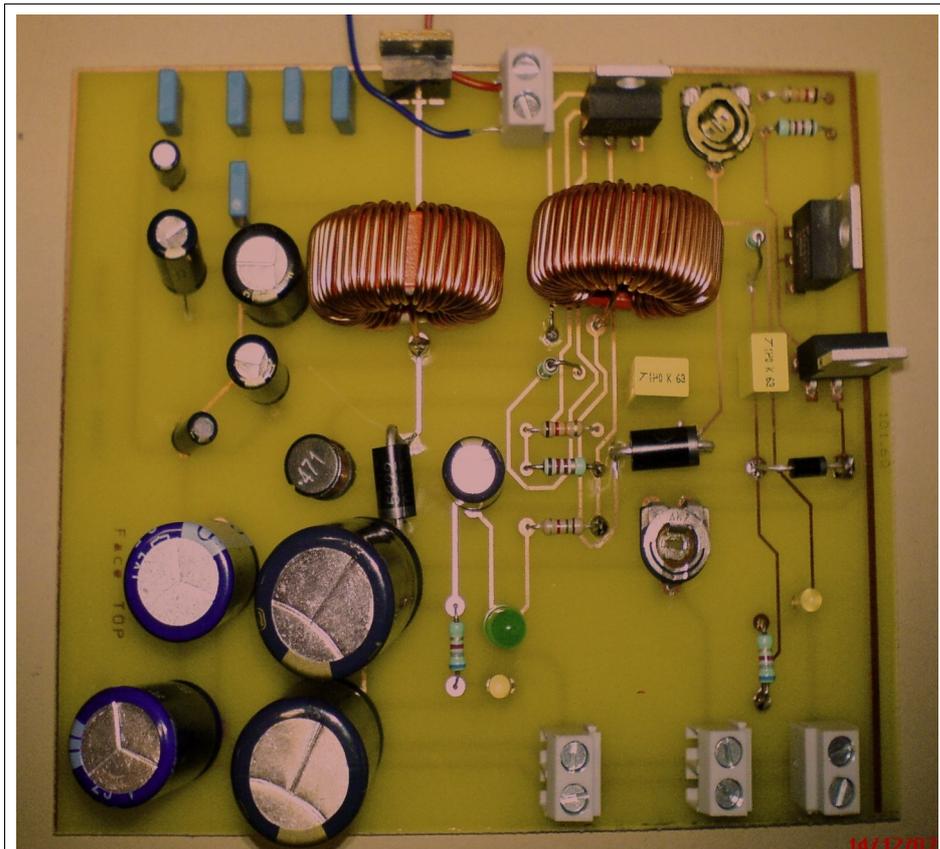


## Rapport de projet tutoré




### **Alimentation**

**12 V vers +5 V et 2 x +15 V**

TRAN Tien Thanh  
2<sup>ème</sup> Année - Q2  
Promotion 2006 / 2008

Enseignant:  
M. Thierry LEQUEU

## Rapport de projet tutoré

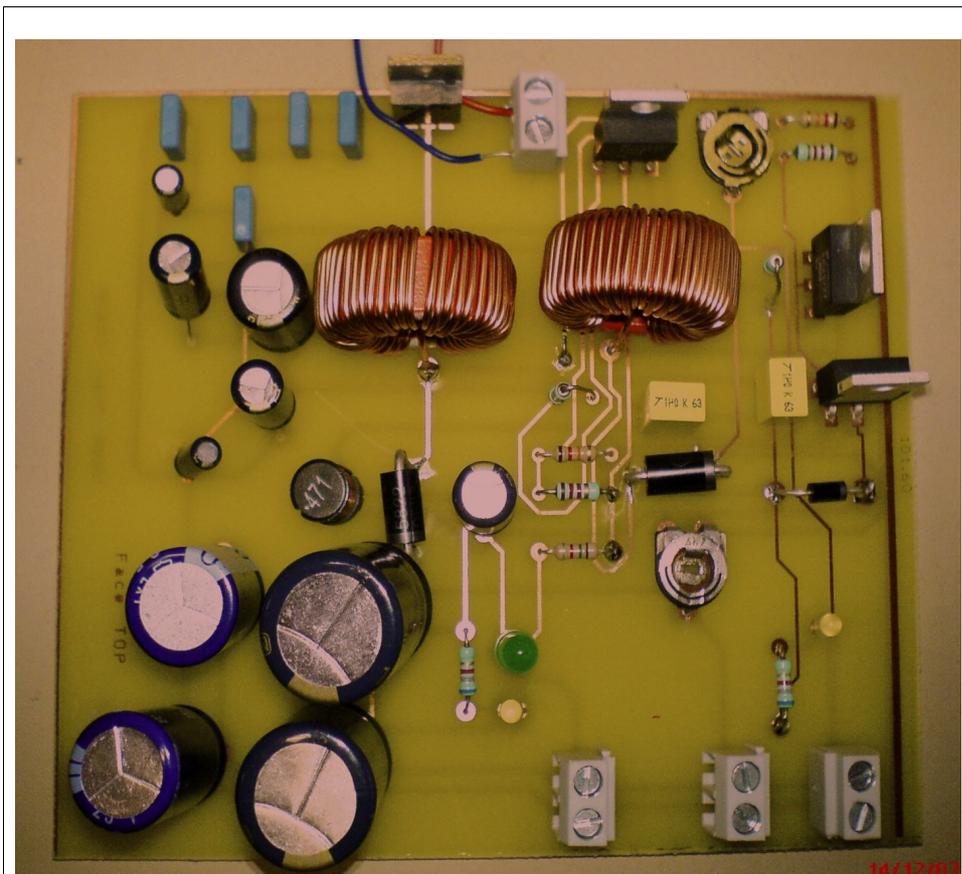

### **Alimentation**

**12 V vers +5 V et 2 tensions +15 V**

TRAN Tien Thanh  
2<sup>ème</sup> Année - Q2  
Promotion 2006 / 2008

Enseignant:  
M. Thierry LEQUEU

# Sommaire

|  |    |
|--|----|
| Introduction.....  | 4  |
| A.Schéma de la carte d'alimentation.....   | 7  |
| B.Calcul théorique des valeurs des composants .....                                  | 9  |
| 1. Objectif:.....  | 9  |
| 2. Régulateur de tension:.....   | 9  |
| 2.1. Présentation: .....   | 9  |
| 2.2. LM 2575T-05 : .....   | 10 |
| a) Calcul de l'inductance L1 : .....   | 10 |
| b) Calcul de la capacité de sortie : .....   | 11 |
| c) Choix de la Diode D : .....   | 11 |
| d) Choix du condensateur d'entrée CIN : .....  | 11 |
| 2.3. LM2577T_ADJ : .....   | 11 |
| a) Calcul de la résistance de sortie : .....   | 12 |
| b) Calcul de l'inductance:.....  | 13 |
| c) La valeur maximale de Rc ( R10 ) : .....  | 15 |
| d) Calcul de la valeur minimale COUT: en utilisant les deux formules suivantes:..... | 15 |
| e) Calcul de la valeur minimale Cc : .....   | 16 |
| C.Fabrication de la carte:.....  | 16 |
| Processus de fabrication de la carte:.....   | 17 |
| & Tests sur la carte. ....   | 17 |
| & Point de tests : .....   | 17 |
| & Résultat des tests.....  | 17 |
| Conclusion.....  | 18 |
| ANNEXE.....  | 20 |
| Annexe1 : Tableau de calcul .....  | 20 |
| Annexe 2 : Nomenclature.....   | 21 |
| Annexe 3 : Régulateur LM2577.....  | 22 |
| Annexe 4 : Régulateur LM 2575.....   | 28 |
| Annexe 5 : Diode 1N5822.....   | 35 |
| Annexe 6 : Diode MBR 2045CT.....   | 36 |
| Annexe 6 : Implantation des composants.....  | 37 |
| Bibliographie.....   | 40 |

# Introduction

Ce projet répond au besoin du club e-Kart d u département GEII. Celui-ci a besoin d'une alimentation 2x +15V et +5V pour alimenter les afficheurs et les différentes cartes électroniques de commande. La source d'entrée de cette alimentation est une batterie de voiture de 12V. Il existe plusieurs méthodes pour réaliser cette fonction. Ici, j'utiliserai des régulateurs de tension de type LM xxxx qui fournissent une tension de référence fixe, donc on peut obtenir des tensions comme on le souhaite auxquels il faudra ajouter quelques composants extérieurs.

# Cahier des charges

- ♦ A partir d'une batterie 12V qui alimente le circuit. La tension d'entr e est typiquement de 12 V mais elle peut varier entre 10 V et 14 V sans qu'il y ait de variation de la tension de sortie. On doit fournir 3 tensions de sorties : une tension + 5V pour alimenter les micro-contr leur et deux tensions + U r glable de 15   17V pour alimenter les afficheurs 7 segments.

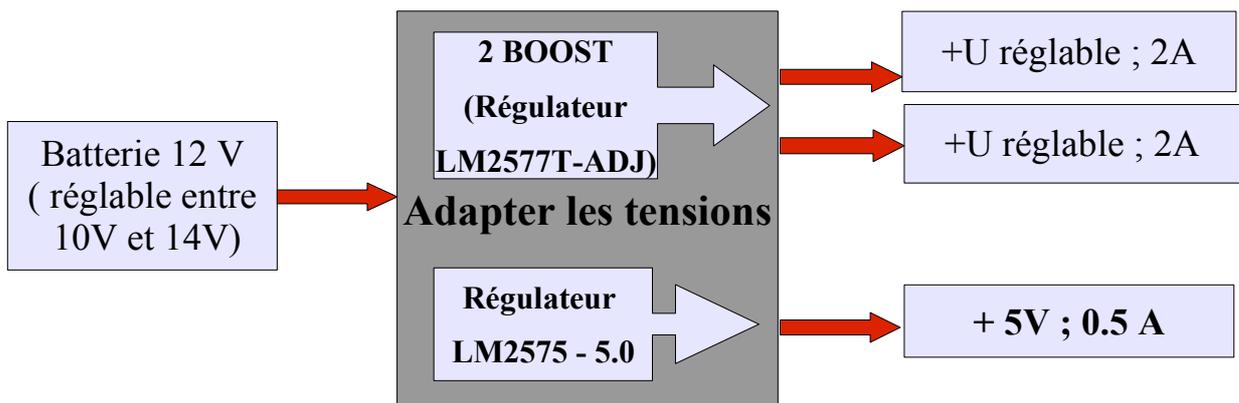


Figure 1 : Sch ma fonctionnel

# Planning prévisionnel

| Tâches  | 37                    | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45            | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 01 | 02 |  |
|---|-----------------------|----|----|----|----|----|----|----|---------------|----|----|----|----|----|----|----|----|----|--|
| Lecture du sujet proposé  |                       | ■  |    |    |    |    |    |    |               |    |    |    |    |    |    |    |    |    |  |
| Le planning prévisionnel & le cahier des charge                   |                       |    | ■  |    |    |    |    |    |               |    |    |    |    |    |    |    |    |    |  |
| la formation Orcad Capture et Layout                              |                       |    |    | ■  |    |    |    |    |               |    |    |    |    |    |    |    |    |    |  |
| Trouver toutes les fonctions des composants nécessaires au projet |                       |    |    |    | ■  |    |    |    |               |    |    |    |    |    |    |    |    |    |  |
| Calculer les valeurs des composants                               |                       |    |    |    |    | ■  | ■  | -- |               |    |    |    |    |    |    |    |    |    |  |
| Faire le typon  |                       |    |    |    |    |    |    |    | ■             |    |    |    |    |    |    |    |    |    |  |
| Fabrication de la carte   |                       |    |    |    |    |    |    |    |               |    | ■  | ■  |    |    |    |    |    |    |  |
| Tester et réparer la carte  |                       |    |    |    |    |    |    |    |               |    |    |    | ■  |    |    |    |    |    |  |
| Préparation du dossier  |                       |    |    |    |    |    |    |    |               |    |    |    |    | ■  |    |    |    |    |  |
| Oral  |                       |    |    |    |    |    |    |    |               |    |    |    |    |    | ■  | -- | -- | ■  |  |
|   |                       |    |    |    |    |    |    |    |               |    |    |    |    |    |    |    |    | ■  |  |
| ■   | Planning prévisionnel |    |    |    |    |    |    | ■  | Planning réel |    |    |    |    |    |    |    |    |    |  |

Figure 2 : Planning prévisionnel et réel

# A. Schéma de la carte d'alimentation

- On aura 2 schémas : le schéma général et le schéma du Boost.

## Schéma général :

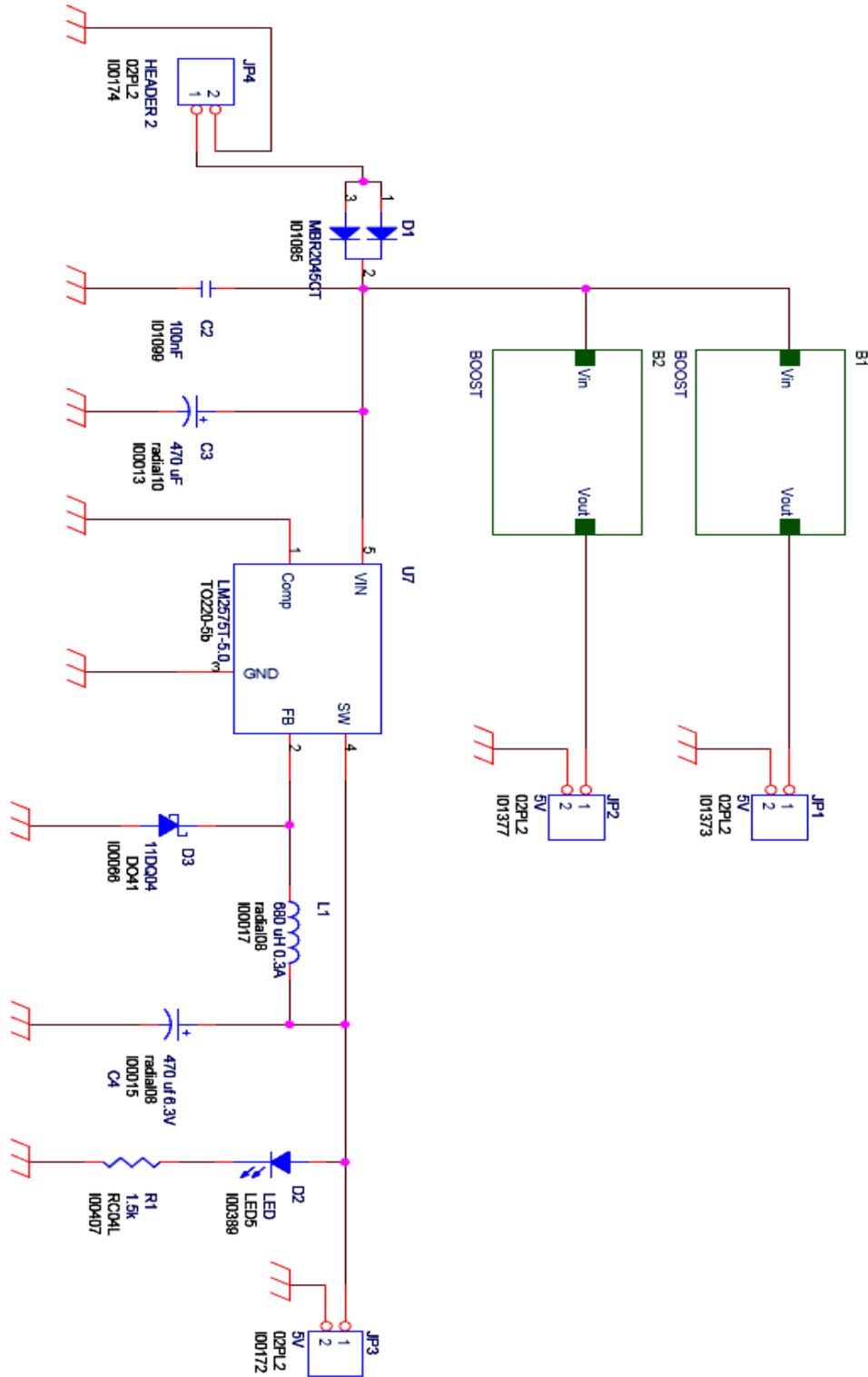


Figure 3 Schéma général

## Schéma du BOOST :

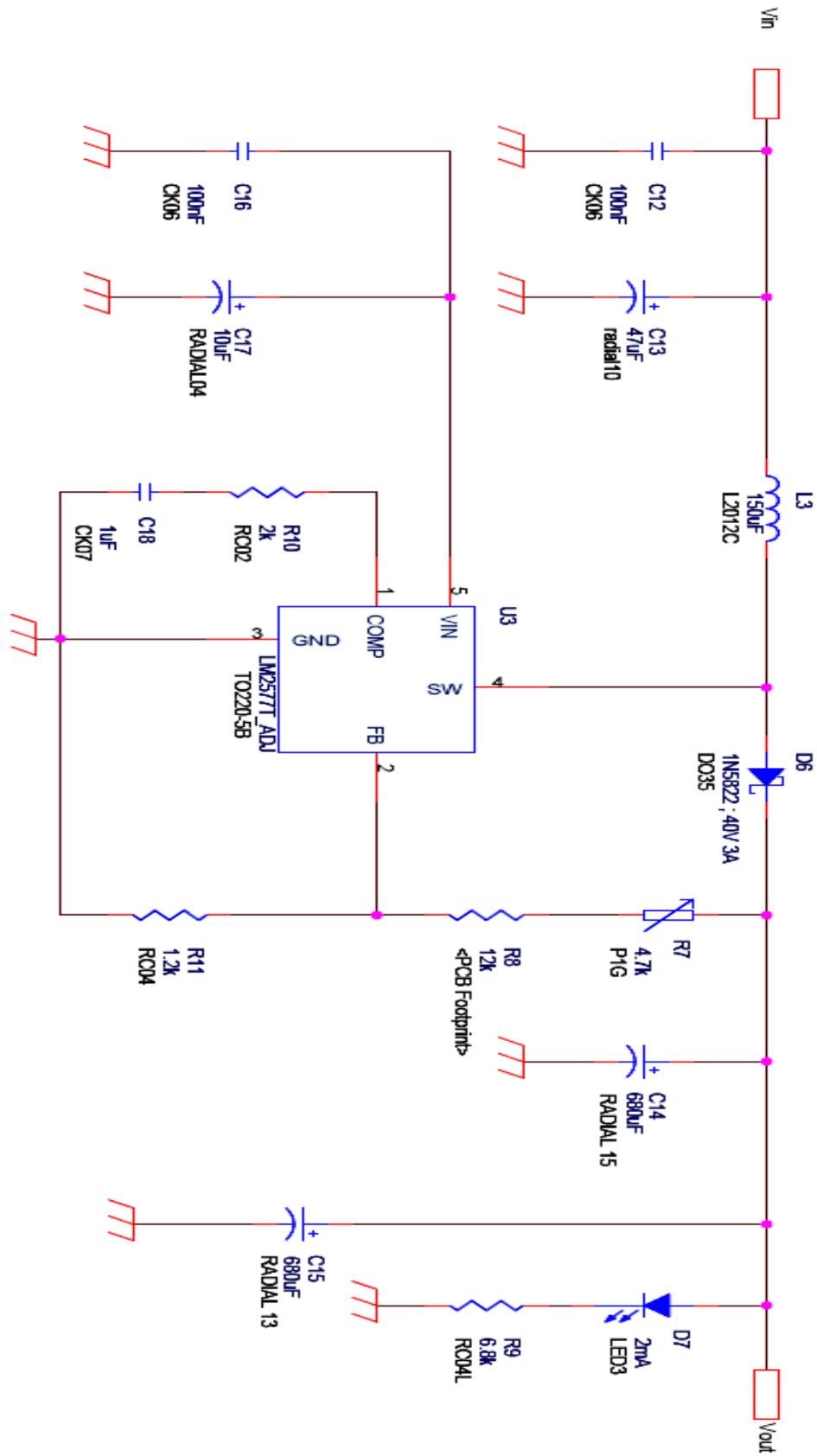


Figure 4 Schéma BOOST

## **B. Calcul théorique des valeurs des composants**

### **1. Objectif:**

Les différentes études proposées ont pour but une parfaite compréhension du fonctionnement des différents composants présents sur le schéma. Cela revient à étudier les différents points:

- + régulation de tension (2577T\_ADJ ; 2575T\_5.0)
- + calcul du condensateur + choix de l'inductance

### **2. Régulateur de tension:**

#### **2.1. Présentation:**

- Un régulateur de tension est un élément qui permet de stabiliser une tension à une valeur fixe. Un régulateur de tension peut être composé d'un ensemble de composants classiques ( résistance, diodes zener et transistor par exemple), mais il peut aussi être de type " intégré " et contenir tout ce qu'il faut dans un seul et même boîtier, pour faciliter son usage.
- Tout régulateur est capable de supporter une tension d'entrée jusqu'à une certaine valeur. De même, tout régulateur est capable de délivrer un courant maximal ( $I_{LOAD\ max}$ ).

## 2.2. LM 2575T-05 :

On va étudier le schéma général.

- LM 2575T-05 est un régulateur de tension fixe qui fournit une tension de sortie 5 V.
- Type d'application :

### Typical Application (Fixed Output Voltage Versions)

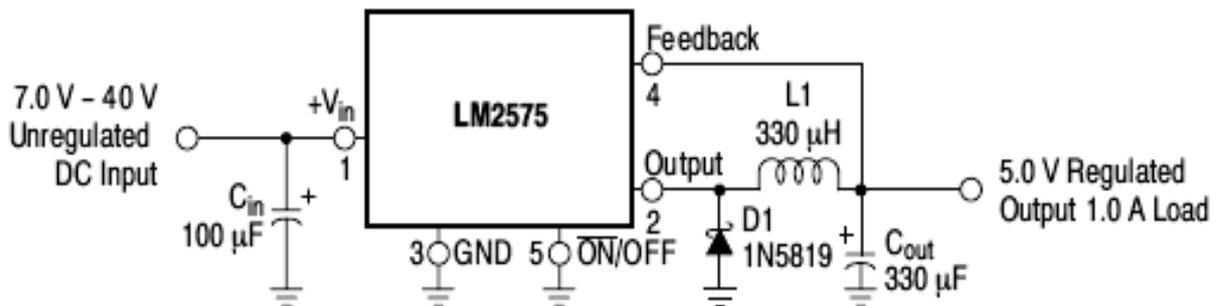


Figure 5: Schéma d'application du régulateur LM2575T-05

- D'après la documentation technique:

### a) Calcul de l'inductance L1 :

$$E \times T = (V_{in} - V_{out}) \frac{V_{out}}{V_{on}} \times \frac{10^6}{F[\text{Hz}]} [\text{V} \times \mu\text{s}]$$

Sur notre schéma, on a  $V_{IN} = 12 \text{ V}$ ,  $V_{OUT} = 5 \text{ V}$ ,  $F = 52 \text{ kHz}$ .

Application numérique : on a  $E.T = 56 \text{ V} \mu\text{s}$

En pratique, on prend

$$L = 680 \mu\text{H} \text{ et } I_L = 0.32 \text{ A}$$

### **b) Calcul de la capacité de sortie :**

$$C_{out} \geq 7.785 \frac{V_{in(max)}}{V_{out} \times L [\mu H]} \quad (\text{ en mF } )$$

$$\begin{aligned} \Rightarrow C_{OUT} (\text{min}) &= ( 7.785 \times 14 ) / ( 5 \times 680 ) = 0.032 \text{ mF} \\ &= 32 \mu\text{F} \end{aligned}$$

$$\text{Et } V_{C_{OUT}} \simeq 1.5 * V_{OUT} = 1.5 * 5 = 7.5 \text{ V}$$

En pratique, on prend

$$C4 = C_{OUT} = 470 \mu\text{F} \quad 6,3 \text{ V}$$

### **c) Choix de la Diode D :**

$$. I_D > 1.2 * I_{LOAD(max)} = 1.2 * 0.32 = 0.384 \text{ A}$$

$$. V_D > 1.25 * V_{IN(max)} = 1.25 * 14 = 17.5 \text{ V}$$

$\Rightarrow$  On choisit D3 :

$$1\text{N}5819 ( 40\text{V}, 1\text{A}). \quad \text{ou } 11\text{DQ}04.$$

### **d) Choix du condensateur d'entrée $C_{IN}$ :**

$$C_{IN} = C2 // C3$$

En pratique, pour le découplage HF on prend  $C2 = 100 \text{ nF}, 63 \text{ V}$

et pour le découplage BF.  $C3 = 470 \mu\text{F}, 25 \text{ V}$

### **2.3. LM2577T\_ADJ :**

On va étudier le schéma du BOOST.

LM2577T\_ADJ est un régulateur ajustable.

- Les régulateurs ajustables ont été conçus afin de pouvoir fournir une tension de sortie pouvant prendre une valeur quelconque dans une plage bien déterminée, et dont la valeur peut être réglée facilement. La plupart du temps, la tension de sortie d'un régulateur de tension ajustable est déterminée par la valeur de deux résistances additionnelles.

- **Type d'application :**

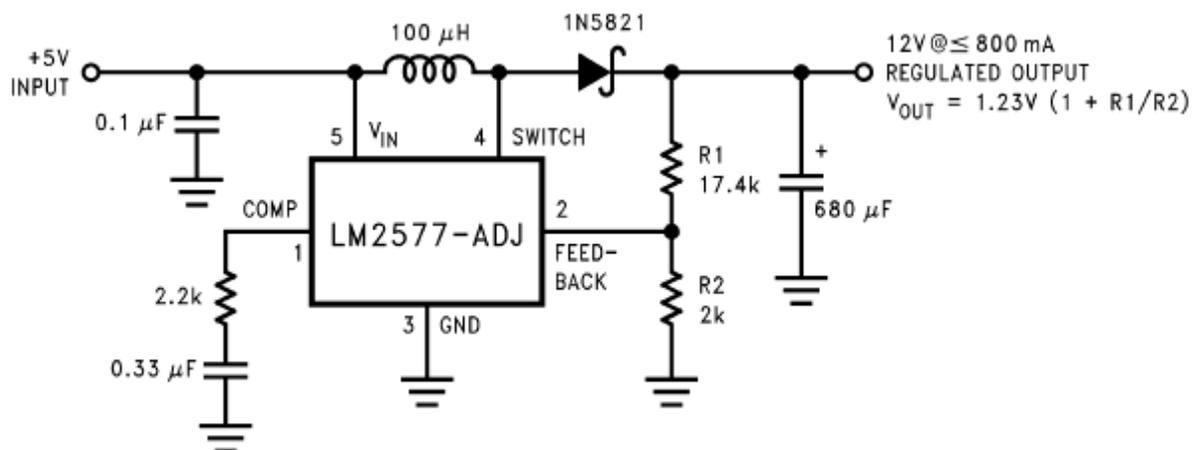


Figure 6 : Schéma d'application du régulateur LM2577T-ADJ

- D'après la documentation technique:

**a) Calcul de la résistance de sortie :**

Pour un LM 2577T\_ADJ, la tension de sortie est donnée par :

$$V_{out} = 1,23 ( 1 + R1 / R2 )$$

Soit  $R1 = R2 ( V_{out} / 1,23 - 1 )$

1,23 est la valeur de la tension de référence (Feed Back) en volts.

On a besoin de  $V_{OUT}$  variable entre 15V et 17V et  $R2 = R1 = 1,2 \text{ kOhm}$

D'après le tableau de calcul, on a  $R_{1\min} = 13434 \text{ Ohm}$  pour  $V_{\text{OUT}} = 15 \text{ V}$

$R_{1\max} = 15385 \text{ Ohm}$  pour  $V_{\text{OUT}} = 17 \text{ V}$

En pratique, pour faire varier la tension de sortie, on remplace la résistance  $R_1$  par 2 résistances, dont l'une est variable, en série car  $V_{\text{OUT}}$  est fonction de  $R_1$ . Donc  $R_1 = R_f + R_{aj}$

\*  $R_f$  (fixe) = 12 kOhm \*  $R_{aj} = 4,7 \text{ kOhm}$  (résistance ajustable)

Soit dans le schéma,

$$R_8 = R_f = 12K.Ohm$$

$$R_7 = R_{aj} = 4,7 K.Ohm$$

- Comme  $V_{\text{OUT}}$  dépend de la valeur  $R_{aj}$ ,  $V_{\text{OUT}}$  aura 2 nouvelles valeurs limites :

\*  $R_{aj} = 0 \Rightarrow R_1 = R_f = 12 \text{ kOhm} \Rightarrow V_{\text{OUT min}} = 13,53 \text{ V}$

\*  $R_{aj} = 4,7 \text{ kOhm} \Rightarrow R_1 = R_f + R_{aj} = 16,7 \text{ kOhm} \Rightarrow V_{\text{OUT max}} = 18.35 \text{ V}$

$\Rightarrow$  On peut dire que c'est  $R_1$  et  $R_2$  du schéma précédent qui permettent de "programmer" la tension de sortie. Ici, c'est  $R_8$  ajustable qui fait varier la tension de sortie  $V_{\text{out}}$ .

### b) Calcul de l'inductance:

- La batterie :  $V_{\text{IN min}} = 10 \text{ V}$

$$I_{\text{LOAD(max)}} \leq \frac{2.1A \times V_{\text{IN(min)}}}{V_{\text{OUT}}}$$

$$D_{(\max)} = \frac{V_{\text{OUT}} + V_F - V_{\text{IN(min)}}}{V_{\text{OUT}} + V_F - 0.6V}$$

- D'après le tableau de calcul, on a :  $D_1(\max) = 0.3$  et  $D_2(\max) = 0.49$ , ces 2 valeurs sont inférieures à 0.85. Donc, on ne peut pas calculer la valeur de l'inductance par la formule suivante :

$$L_{\text{MIN}} = \frac{6.4 (V_{\text{IN(min)}} - 0.6V) (2D_{(\max)} - 1)}{1 - D_{(\max)}} \quad (\mu H)$$

Il nous faut :

- Calculer le produit de Volt \* Time (E.T) qui change la valeur de l'inductance.

$$E \cdot T = \frac{D_{(max)} (V_{IN(min)} - 0.6V) 10^6}{52,000 \text{ Hz}} \quad (V \cdot \mu s)$$


D'après le tableau de calcul, on a : E.T1 = 54,24      E.T2 = 88

- Et calculer le courant d'inductance moyen sous la pleine charge

$$I_{IND,DC} = \frac{1.05 \times I_{LOAD(max)}}{1 - D_{(max)}}$$

I<sub>IND,DC1</sub> = 2.33 A  
I<sub>IND,DC2</sub> = 2.33 A

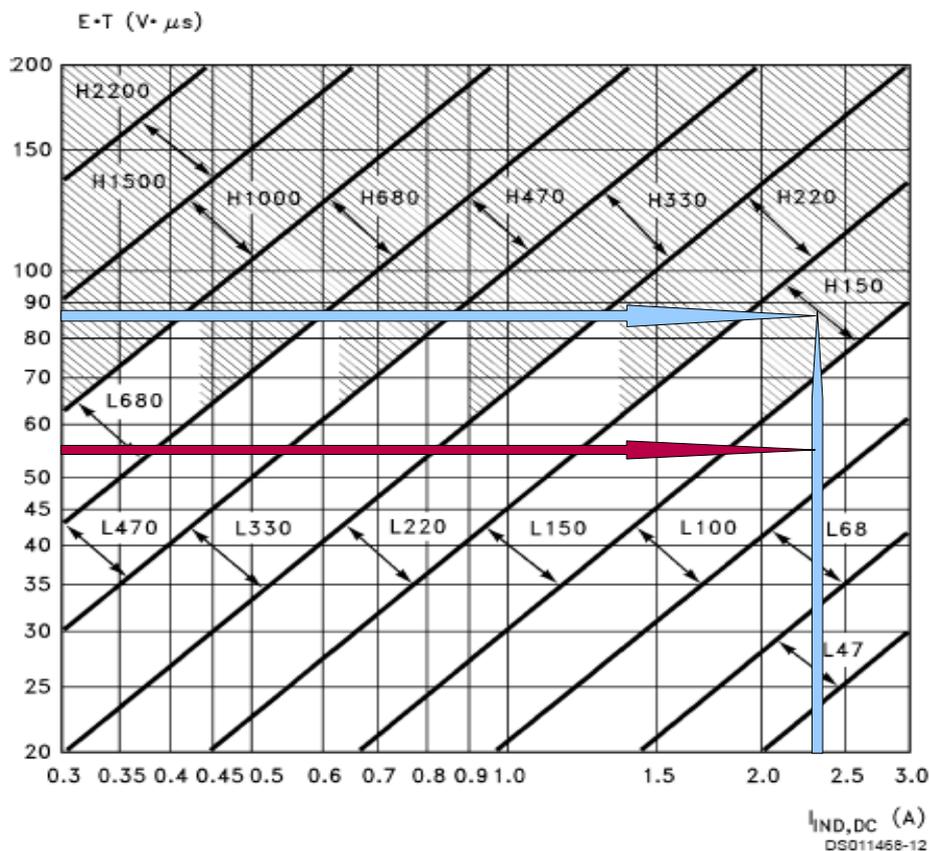En déduire sa valeur en utilisant le tableau suivant:



- On aura 2 valeurs de Lmin: Lmin1 = 100 μH et Lmin2 = 150 μH.

- Si on avait 2 valeurs de  $L_{min}$ , on choisirait la plus grande possible.

==> La valeur d'inductance :

$$L = 150 \text{ (}\mu\text{H)}$$

**c) La valeur maximale de  $R_c$  (  $R_{10}$  ) :**

$$R_c \leq \frac{750 \times I_{LOAD(max)} \times V_{OUT}^2}{V_{IN(min)}^2}$$

D'après le tableau de calcul, on a :  $R_{c1} = 2131\text{Ohm}$  et  $R_{c2} = 2890 \text{ Ohm}$

En pratique, on prend

$$R_{10} = R_c = 2 \text{ K.Ohm}$$

**d) Calcul de la valeur minimale  $C_{OUT}$ : en utilisant les deux**

**formules suivantes:**

$$C_{OUT} \geq \frac{V_{IN(min)} \times R_c \times (V_{IN(min)} + (3.74 \times 10^5 \times L))}{487,800 \times V_{OUT}^3}$$

$$C_{OUT} \geq \frac{0.19 \times L \times R_c \times I_{LOAD(max)}}{V_{IN(min)} \times V_{OUT}}$$

La plus grande de ces deux valeurs est la valeur minimale qui garantit la stabilité.

D'après le tableau de calcul, on a :  $C_{out} = 1.09 \text{ mF}$

Sur le schéma,  $C_{out} = C_{14} // C_{15} = C_{14} + C_{15}$

Donc, en pratique, on prend  $C14 = C15 = 1000 \mu\text{F}, 25\text{V}$

$$\Rightarrow \text{Cout} = 2 \text{ mF}$$

### e) Calcul de la valeur minimale Cc :

$$C_C \geq \frac{58.5 \times V_{\text{OUT}}^2 \times C_{\text{OUT}}}{R_C^2 \times V_{\text{IN}(\text{min})}}$$

D'après le tableau de calcul, on va choisir Cc ayant la plus grande valeur,

$$C_C = 670 \text{ nF}$$

En pratique, on utilise

$$C18 = C_C = 1 \mu\text{F}, 63\text{V}.$$

## 2. Choix de la Diode :

En pratique, on a  $V_{\text{OUT}} = 18.35\text{V}$  et  $I_{\text{LOAD max}} = 1.552 > 1 \text{ A}$

$$V_{\text{RRM}} \geq V_{\text{OUT}} * 1.5 = 18.35 * 1.5 = 27.5 \text{ V}$$

$$I_{\text{F(AV)}} = I_{\text{LOAD (max)}} * 1.5 = 1.552 * 1.5 = 2.33 \text{ A}$$

$\Rightarrow$  On va prendre :  $D : 1\text{N}5822$

ses caractéristiques :  $V = 40 \text{ V}$  et  $I = 3 \text{ A}$

## **C. Fabrication de la carte:**

Il nous faut faire le typon en double face avec les logiciels :

- Orcard pour simuler le schéma de la carte.
- Layout pour créer le typon de la carte.
- La liste des composants que j'ai utilisé pour ce circuit est présentée à l'annexe II.

## **Processus de fabrication de la carte:**

J'ai rencontré quelques problèmes lorsque j'ai soudé les composants.

- il y a quelques pattes de composants trop gros ( Diode 1N5822 par exemple ).
- Ce circuit est soudé en double faces donc, j'ai eu du mal à souder la deuxième face car les pattes des composants étaient trop petites.

### **Tests sur la carte.**

- Appareils de mesure nécessaires : un oscilloscope, un générateur
- Alimenter le circuit : une tension d'entrée 12 V continue.

### **Point de tests :**

- Les tensions de référence des régulateurs de tension LM2577 et LM2575.
- La tension de sortie + 5 V.
- La tension de sortie + 15 V variable.

### **Résultat des tests**

- J'ai obtenu 2 tensions de sortie + 11, 8 V (avec les différentes valeurs de R ajustable) correspondant aux 2 sorties + 15V variable.
- je n'ai rien obtenu à la sortie + 5V : le voltmètre affichait 0V

## Conclusion

Pour créer une tension continue dont la valeur est de quelques dizaines de volts, à partir d'une source de tension continue ( une batterie par exemple) environ quelques dizaines de volts, on peut utiliser les régulateurs de tension qui fournissent une tension de référence fixe. La tension de sortie est fixée en fonction de la valeur des résistances de sortie.

On peut également dire que ce circuit est un convertisseur de tension continu - continu ( DC – DC ). Je n'ai pas eu assez de temps pour rechercher la panne de ma carte. Après avoir vérifié le schéma et le typon sur orcard, je me suis aperçu que j'ai oublié une piste et j'ai inversé les broches 1 et 5 du régulateur LM2575T-05.

Bien que ce projet était plutôt simple, je n'ai pas eu le temps pour le terminer car j'étais tout seul à travailler dessus et le logiciel Orcad m'a fait perdre beaucoup de temps. D'autre part j'ai des difficultés de compréhension de la langue française et cela m'a gêné dans l'organisation de mon projet.

## **Index des illustrations**

|  |    |
|--|----|
| Figure 1 : Schéma fonctionnel.....                             | 5  |
| Figure 2 : Planning prévisionnel et réel.....                  | 6  |
| Figure 3 Schéma général.....                                   | 7  |
| Figure 4 Schéma BOOST.....                                     | 8  |
| Figure 5: Schéma d'application du régulateur LM2575T-05.....   | 10 |
| Figure 6 : Schéma d'application du régulateur LM2577T-ADJ..... | 12 |
| Figure 7 : Tableau de calcul.....                              | 20 |
| Figure 8: Plan de perçage.....                                 | 37 |
| Figure 9: Emplacement des composants.....                      | 37 |
| Figure 10: Typon complet.....                                  | 38 |
| Figure 11 : Typon de la face de dessus(TOP).....               | 39 |
| Figure 12 : Typon de la face de-dessous (BOTTOM).....          | 39 |

# ANNEXE

## Annexe1 : Tableau de calcul

|   |          |          |      |
|---|----------|----------|------|
| $V_s =$                                 | 10       | 17       | V    |
| $V_{ref} =$                             | 1.23     | 1.23     | V    |
| $R_2 =$                                 | 1200     | 1200     | Ohms |
| $R_1 =$                                 | 13434.10 | 10380.37 | Ohms |
| <b>Choix de <math>R_1</math> :</b>      |          |          |      |
| $R_1 =$                                 | 12000    | 16700    | Ohms |
| <b><math>V_{out} =</math></b>           | 13.03    | 18.30    | V    |
| <b><math>V_{in(min)} =</math></b>       | 10       | 10       | V    |
| <b><math>I_{load(max)} =</math></b>     | 1.00     | 1.14     | A    |
| <b><math>V_F =</math></b>               | 0.5      | 0.5      | V    |
| <b><math>D(max) =</math></b>            | 0.3      | 0.49     |      |
| <b><math>E.T =</math></b>               | 04.24    | 88       | V.us |
| <b><math>I_{ind,dc}</math></b>          | 2.33     | 2.33     | A    |
| <b>Choix de l'inductance :</b>          |          |          |      |
| <b><math>L_{min}</math></b>             | 100      | 100      | UH   |
| <b>Calcul de <math>R_c =</math></b>     | 2130.98  | 2889.73  | Ohms |
| <b>Choix de <math>R_c:</math></b>       | 2000     | 2000     | Ohms |
| calcul du Cout                          |          |          |      |
| $C_{out1} =$                            | 0.60     | 0.36     | mF   |
| $C_{out2} =$                            | 1.09     | 0.44     | mF   |
| <b>Choix de Cout min:</b>               | 1.36     | 1.36     | mF   |
| <b>Calcul de <math>C_c</math> min =</b> | 364      | 670      | nF   |
| <b>Choix de <math>C_c</math> min:</b>   | 680      | 680      | nF   |
| <b>Choix de <math>C_{in}:</math></b>    |          |          |      |
| $C_{in} = C_1 // C_2$                   |          |          |      |
| $C_1 =$                                 | 100      | 100      | nF   |
| $C_2 =$                                 | 47       | 47       | uF   |

Figure 7 : Tableau de calcul


## Annexe 2 : Nomenclature

*Liste de composants .*

*Remarque : Les valeurs des composants en pratique peut être différentes aux valeurs prévues*

| N° | Quantité | Référence        | Désignation   | Prix en Euros | Total en Euros |
|----|----------|------------------|---------------|---------------|----------------|
| 1  | 5        | C2,C5,C9,C12,C16 | 100 nF        | 0,1755        | 0,8775         |
| 2  | 2        | C14, C15         | 680µF , 25V   | 0,564         | 1,128          |
| 3  | 2        | C7, C8           | 680µF , 25V   | 0,564         | 1,128          |
| 4  | 2        | C18, C11         | 1 µF , 63 V   | 0,462         | 0,924          |
| 5  | 2        | C6, C13          | 47 µF, 25 V   | 0,158         | 0,316          |
| 6  | 2        | C10, C17         | 10 µF, 50 V   | 0,136         | 0,272          |
| 7  | 2        | L2, L3           | 150 µH,       | 2,30          | 4,6            |
| 8  | 1        | L1               | 680 µH, 0,3A  | 1,94          | 1,94           |
| 9  | 1        | C4               | 470 µF ; 6,3V | 0,27          | 0,27           |
| 10 | 2        | R7 , R2          | 4.7 kOhm      |               |                |
| 11 | 2        | R8, R3           | 12 kOhm       | 0,0252        | 0,0504         |
| 12 | 2        | R11, R6          | 1.2 kOhm      | 0,01411       | 0,02822        |
| 13 | 2        | R9, R4           | 6.8 kOhm      | 0,01411       | 0,02822        |
| 14 | 1        | R1               | 1.5 kOhm      | 0,042         | 0,042          |
| 15 | 2        | R5, R10          | 2 kOhm        | 0,074         | 0,148          |
| 16 | 1        | D2               | 2 mA          | 0,158         | 0,158          |
| 17 | 2        | D5, D7           | Led           | 0,158         | 0,316          |
| 18 | 2        | D6, D4           | 1N5822        | 0,57          | 1,14           |
| 19 | 1        | D3               | 1N5819        | 1,11          | 1,11           |
| 20 | 1        | U1               | LM2575T-5.0   | 1,91          | 1,91           |
| 21 | 2        | U2, U3           | LM2577T-ADJ   | 8,85          | 17,7           |
| 22 | 2        | JP1,JP2          | +15 V         |               |                |
| 23 | 1        | JP 3             | +5 V          |               |                |
| 24 | 1        | JP4              | 12 V          |               |                |
| 25 | 1        | D1               | MBR2045CT     |               |                |
| 26 | 1        | C3               | 470 µF, 25V   | 0,452         | 0,452          |
|    |          |                  |               | TOTAL         |                |

# Annexe 3 : Régulateur LM2577

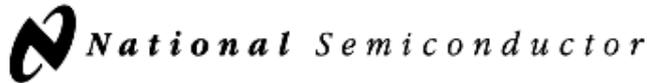

June 1999

## LM1577/LM2577 Series SIMPLE SWITCHER® Step-Up Voltage Regulator

### General Description

The LM1577/LM2577 are monolithic integrated circuits that provide all of the power and control functions for step-up (boost), flyback, and forward converter switching regulators. The device is available in three different output voltage versions: 12V, 15V, and adjustable.

Requiring a minimum number of external components, these regulators are cost effective, and simple to use. Listed in this data sheet are a family of standard inductors and flyback transformers designed to work with these switching regulators.

Included on the chip is a 3.0A NPN switch and its associated protection circuitry, consisting of current and thermal limiting, and undervoltage lockout. Other features include a 52 kHz fixed-frequency oscillator that requires no external components, a soft start mode to reduce in-rush current during start-up, and current mode control for improved rejection of input voltage and output load transients.


### Features

- Requires few external components
- NPN output switches 3.0A, can stand off 65V
- Wide input voltage range: 3.5V to 40V
- Current-mode operation for improved transient response, line regulation, and current limit
- 52 kHz internal oscillator
- Soft-start function reduces in-rush current during start-up
- Output switch protected by current limit, under-voltage lockout, and thermal shutdown

### Typical Applications

- Simple boost regulator
- Flyback and forward regulators
- Multiple-output regulator

### Typical Application

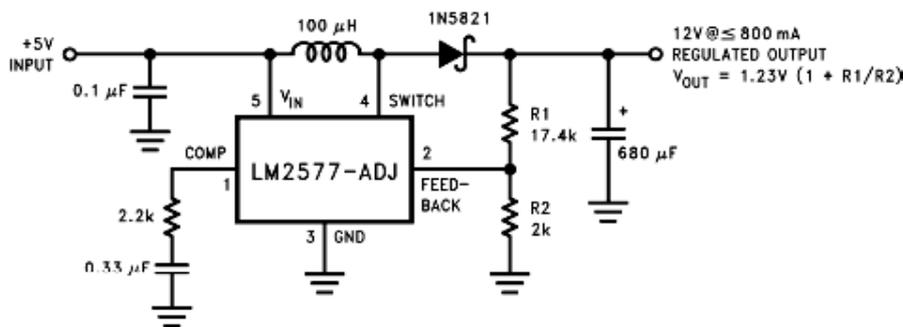

Note: Pin numbers shown are for TO-220 (T) package.

DS011468-1

### Ordering Information

| Temperature Range               | Package Type           | Output Voltage |                |                 | NSC Package Drawing | Package |
|---------------------------------|------------------------|----------------|----------------|-----------------|---------------------|---------|
|                                 |                        | 12V            | 15V            | ADJ             |                     |         |
| -40°C ≤ T <sub>A</sub> ≤ +125°C | 24-Pin Surface Mount   | LM2577M-12     | LM2577M-15     | LM2577M-ADJ     | M24B                | SO      |
|                                 | 16-Pin Molded DIP      | LM2577N-12     | LM2577N-15     | LM2577N-ADJ     | N16A                | N       |
|                                 | 5-Lead Surface Mount   | LM2577S-12     | LM2577S-15     | LM2577S-ADJ     | TS5B                | TO-263  |
|                                 | 5-Straight Leads       | LM2577T-12     | LM2577T-15     | LM2577T-ADJ     | T05A                | TO-220  |
|                                 | 5-Bent Staggered Leads | LM2577T-12     | LM2577T-15     | LM2577T-ADJ     | T05D                | TO-220  |
| -55°C ≤ T <sub>A</sub> ≤ +150°C | 4-Pin TO-3             | Flow LB03      | Flow LB03      | Flow LB03       | K04A                | TO-3    |
|                                 |                        | LM1577K-12/883 | LM1577K-15/883 | LM1577K-ADJ/883 |                     |         |

SIMPLE SWITCHER® is a registered trademark of National Semiconductor Corporation.

## Application Hints (Continued)

### STEP-UP (BOOST) REGULATOR

Figure 4 shows the LM1577-ADJ/LM2577-ADJ used as a Step-Up Regulator. This is a switching regulator used for producing an output voltage greater than the input supply voltage. The LM1577-12/LM2577-12 and LM1577-15/LM2577-15 can also be used for step-up regulators with 12V or 15V outputs (respectively), by tying the feedback pin directly to the regulator output.

A basic explanation of how it works is as follows. The LM1577/LM2577 turns its output switch on and off at a frequency of 52 kHz, and this creates energy in the inductor (L). When the NPN switch turns on, the inductor current charges up at a rate of  $V_{IN}/L$ , storing current in the inductor. When the switch turns off, the lower end of the inductor flies above  $V_{IN}$ , discharging its current through diode (D) into the output capacitor ( $C_{OUT}$ ) at a rate of  $(V_{OUT} - V_{IN})/L$ . Thus, energy stored in the inductor during the switch on time is transferred to the output during the switch off time. The output voltage is controlled by the amount of energy transferred which, in turn, is controlled by modulating the peak inductor current. This is done by feeding back a portion of the output voltage to the error amp, which amplifies the difference between the feedback voltage and a 1.230V reference. The error amp output voltage is compared to a voltage proportional to the switch current (i.e., inductor current during the switch on time).

The comparator terminates the switch on time when the two voltages are equal, thereby controlling the peak switch current to maintain a constant output voltage.

Voltage and current waveforms for this circuit are shown in Figure 5, and formulas for calculating them are given in Figure 6.


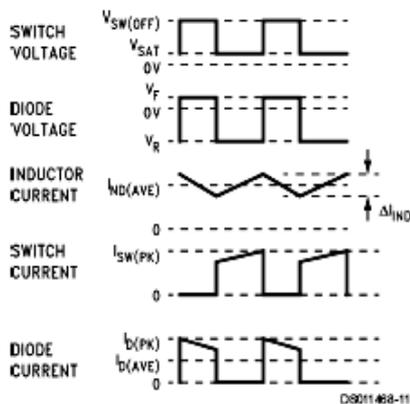


FIGURE 5. Step-Up Regulator Waveforms

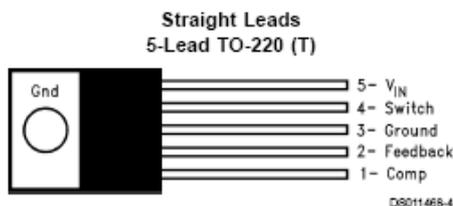

$V_F$  = Forward Biased Diode Voltage

$I_{LOAD}$  = Output Load Current

FIGURE 6. Step-Up Regulator Formulas

### STEP-UP REGULATOR DESIGN PROCEDURE

The following design procedure can be used to select the appropriate external components for the circuit in Figure 4, based on these system requirements.

Given:

$V_{IN(min)}$  = Minimum input supply voltage

$V_{OUT}$  = Regulated output voltage

$I_{LOAD(max)}$  = Maximum output load current

Before proceeding any further, determine if the LM1577/LM2577 can provide these values of  $V_{OUT}$  and  $I_{LOAD(max)}$  when operating with the minimum value of  $V_{IN}$ . The upper limits for  $V_{OUT}$  and  $I_{LOAD(max)}$  are given by the following equations.

$$V_{OUT} \leq 60V$$

$$\text{and } V_{OUT} \leq 10 \times V_{IN(min)}$$

$$I_{LOAD(max)} \leq \frac{2.1A \times V_{IN(min)}}{V_{OUT}}$$

These limits must be greater than or equal to the values specified in this application.

#### 1. Inductor Selection (L)

A. Voltage Options:

1. For 12V or 15V output

Straight Leads  
5-Lead TO-220 (T)

5-  $V_{IN}$   
4- Switch  
3- Ground  
2- Feedback  
1- Comp

Order Number LM2577T-12, LM2577T-15,  
or LM2577T-ADJ  
See NS Package Number T05A

## Application Hints (Continued)

From Figure 7 (for 12V output) or Figure 8 (for 15V output), identify inductor code for region indicated by  $V_{IN(min)}$  and  $I_{LOAD(max)}$ . The shaded region indicates conditions for which the LM1577/LM2577 output switch would be operating beyond its switch current rating. The minimum operating voltage for the LM1577/LM2577 is 3.5V.

From here, proceed to step C.

### 2. For Adjustable version

#### Preliminary calculations:

The inductor selection is based on the calculation of the following three parameters:

$D_{(max)}$ , the maximum switch duty cycle ( $0 \leq D \leq 0.9$ ):

$$D_{(max)} = \frac{V_{OUT} + V_F - V_{IN(min)}}{V_{OUT} + V_F - 0.6V}$$

where  $V_F = 0.5V$  for Schottky diodes and  $0.8V$  for fast recovery diodes (typically);

$E \cdot T$ , the product of volts x time that charges the inductor:

$$E \cdot T = \frac{D_{(max)} (V_{IN(min)} - 0.6V) 10^6}{52,000 \text{ Hz}} \quad (V \cdot \mu s)$$

$I_{IND,DC}$ , the average inductor current under full load;

$$I_{IND,DC} = \frac{1.05 \times I_{LOAD(max)}}{1 - D_{(max)}}$$

#### B. Identify Inductor Value:

1. From Figure 9, identify the inductor code for the region indicated by the intersection of  $E \cdot T$  and  $I_{IND,DC}$ . This code gives the inductor value in microhenries. The L or H prefix signifies whether the inductor is rated for a maximum  $E \cdot T$  of  $90 V \cdot \mu s$  (L) or  $250 V \cdot \mu s$  (H).

2. If  $D < 0.85$ , go on to step C. If  $D \geq 0.85$ , then calculate the minimum inductance needed to ensure the switching regulator's stability:

$$L_{MIN} = \frac{6.4 (V_{IN(min)} - 0.6V) (2D_{(max)} - 1)}{1 - D_{(max)}} \quad (\mu H)$$

If  $L_{MIN}$  is smaller than the inductor value found in step B1, go on to step C. Otherwise, the inductor value found in step B1 is too low; an appropriate inductor code should be obtained from the graph as follows:

1. Find the lowest value inductor that is greater than  $L_{MIN}$ .
2. Find where  $E \cdot T$  intersects this inductor value to determine if it has an L or H prefix. If  $E \cdot T$  intersects both the L and H regions, select the inductor with an H prefix.

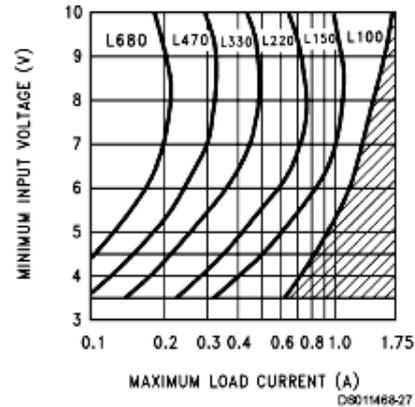


FIGURE 7. LM2577-12 Inductor Selection Guide


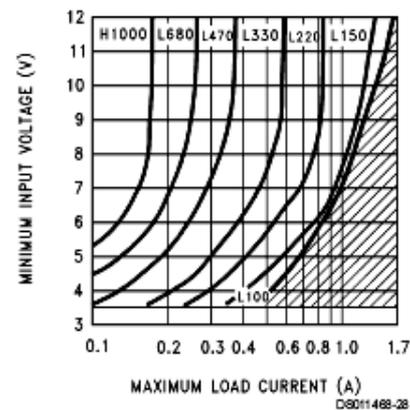


FIGURE 8. LM2577-15 Inductor Selection Guide

## Application Hints (Continued)

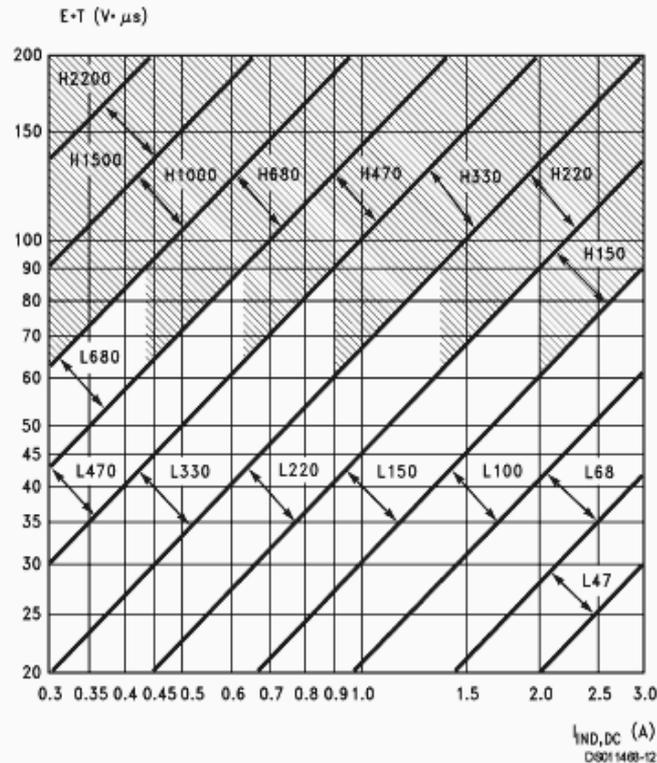

Note: These charts assume that the inductor ripple current is approximately 20% to 30% of the average inductor current (when the regulator is under full load). Greater ripple current causes higher peak switch currents and greater output ripple voltage; lower ripple current is achieved with larger-value inductors. The factor of 20 to 30% is chosen as a convenient balance between the two extremes.

FIGURE 9. LM1577-ADJ/LM2577-ADJ Inductor Selection Graph

- C. Select an inductor from the table of Figure 10 which cross-references the inductor codes to the part numbers of three different manufacturers. Complete specifications for these inductors are available from the respective manufacturers. The inductors listed in this table have the following characteristics:

**AIE:** ferrite, pot-core inductors; Benefits of this type are low electro-magnetic interference (EMI), small physical size, and very low power dissipation (core loss). Be careful not to operate these inductors too far beyond their maximum ratings for  $E \cdot T$  and peak current, as this will saturate the core.

**Pulse:** powdered iron, toroid core inductors; Benefits are low EMI and ability to withstand  $E \cdot T$  and peak current above rated value better than ferrite cores.

**Renco:** ferrite, bobbin-core inductors; Benefits are low cost and best ability to withstand  $E \cdot T$  and peak current above rated value. Be aware that these inductors generate more EMI than the other types, and this may interfere with signals sensitive to noise.

## Application Hints (Continued)

| Inductor Code | Manufacturer's Part Number |            |        |
|---------------|----------------------------|------------|--------|
|               | Schott                     | Pulse      | Renco  |
| L47           | 67126980                   | PE - 53112 | RL2442 |
| L68           | 67126990                   | PE - 92114 | RL2443 |
| L100          | 67127000                   | PE - 92108 | RL2444 |
| L150          | 67127010                   | PE - 53113 | RL1954 |
| L220          | 67127020                   | PE - 52626 | RL1953 |
| L330          | 67127030                   | PE - 52627 | RL1952 |
| L470          | 67127040                   | PE - 53114 | RL1951 |
| L680          | 67127050                   | PE - 52629 | RL1950 |
| H150          | 67127060                   | PE - 53115 | RL2445 |
| H220          | 67127070                   | PE - 53116 | RL2446 |
| H330          | 67127080                   | PE - 53117 | RL2447 |
| H470          | 67127090                   | PE - 53118 | RL1961 |
| H680          | 67127100                   | PE - 53119 | RL1960 |
| H1000         | 67127110                   | PE - 53120 | RL1959 |
| H1500         | 67127120                   | PE - 53121 | RL1958 |
| H2200         | 67127130                   | PE - 53122 | RL2448 |

Schott Corp., (612) 475-1173  
 1000 Parkers Lake Rd., Wayzata, MN 55391  
 Pulse Engineering, (619) 268-2400  
 P.O. Box 12235, San Diego, CA 92112  
 Renco Electronics Inc., (516) 596-6566  
 60 Jeffry Blvd. East, Deer Park, NY 11729

FIGURE 10. Table of Standardized Inductors and Manufacturer's Part Numbers

### 2. Compensation Network ( $R_C$ , $C_C$ ) and Output Capacitor ( $C_{OUT}$ ) Selection

$R_C$  and  $C_C$  form a pole-zero compensation network that stabilizes the regulator. The values of  $R_C$  and  $C_C$  are mainly dependant on the regulator voltage gain,  $I_{LOAD(max)}$ ,  $L$  and  $C_{OUT}$ . The following procedure calculates values for  $R_C$ ,  $C_C$ , and  $C_{OUT}$  that ensure regulator stability. Be aware that this procedure doesn't necessarily result in  $R_C$  and  $C_C$  that provide optimum compensation. In order to guarantee optimum compensation, one of the standard procedures for testing loop stability must be used, such as measuring  $V_{OUT}$  transient response when pulsing  $I_{LOAD}$  (see Figure 15).

A. First, calculate the maximum value for  $R_C$ .

$$R_C \leq \frac{750 \times I_{LOAD(max)} \times V_{OUT}^2}{V_{IN(min)}^2}$$

Select a resistor less than or equal to this value, and it should also be no greater than 3 k $\Omega$ .

B. Calculate the minimum value for  $C_{OUT}$  using the following two equations.

$$C_{OUT} \geq \frac{0.19 \times L \times R_C \times I_{LOAD(max)}}{V_{IN(min)} \times V_{OUT}}$$

and

$$C_{OUT} \geq \frac{V_{IN(min)} \times R_C \times (V_{IN(min)} + (3.74 \times 10^5 \times L))}{487,800 \times V_{OUT}^3}$$

The larger of these two values is the minimum value that ensures stability.

C. Calculate the minimum value of  $C_C$ .

$$C_C > \frac{58.5 \times V_{OUT}^2 \times C_{OUT}}{R_C^2 \times V_{IN(min)}}$$

The compensation capacitor is also part of the soft start circuitry. When power to the regulator is turned on, the switch duty cycle is allowed to rise at a rate controlled by this capacitor (with no control on the duty cycle, it would immediately rise to 90%, drawing huge currents from the input power supply). In order to operate properly, the soft start circuit requires  $C_C \geq 0.22 \mu\text{F}$ .

The value of the output filter capacitor is normally large enough to require the use of aluminum electrolytic capacitors. Figure 11 lists several different types that are recommended for switching regulators, and the following parameters are used to select the proper capacitor.

**Working Voltage (WVDC):** Choose a capacitor with a working voltage at least 20% higher than the regulator output voltage.

**Ripple Current:** This is the maximum RMS value of current that charges the capacitor during each switching cycle. For step-up and flyback regulators, the formula for ripple current is

$$I_{RIPPLE(RMS)} = \frac{I_{LOAD(max)} \times D_{(max)}}{1 - D_{(max)}}$$

Choose a capacitor that is rated at least 50% higher than this value at 52 kHz.

**Equivalent Series Resistance (ESR):** This is the primary cause of output ripple voltage, and it also affects the values of  $R_C$  and  $C_C$  needed to stabilize the regulator. As a result, the preceding calculations for  $C_C$  and  $R_C$  are only valid if ESR doesn't exceed the maximum value specified by the following equations.

$$ESR \leq \frac{0.01 \times V_{OUT}}{I_{RIPPLE(P-P)}} \text{ and } \leq \frac{8.7 \times (10) - 3 \times V_{IN}}{I_{LOAD(max)}}$$

where

$$I_{RIPPLE(P-P)} = \frac{1.15 \times I_{LOAD(max)}}{1 - D_{(max)}}$$

Select a capacitor with ESR, at 52 kHz, that is less than or equal to the lower value calculated. Most electrolytic capacitors specify ESR at 120 Hz which is 15% to 30% higher than at 52 kHz. Also, be aware that ESR increases by a factor of 2 when operating at -20°C.

In general, low values of ESR are achieved by using large value capacitors ( $C \geq 470 \mu\text{F}$ ), and capacitors with high WVDC, or by paralleling smaller-value capacitors.

## Application Hints (Continued)

### 3. Output Voltage Selection (R1 and R2)

This section is for applications using the LM1577-ADJ/LM2577-ADJ. Skip this section if the LM1577-12/LM2577-12 or LM1577-15/LM2577-15 is being used.

With the LM1577-ADJ/LM2577-ADJ, the output voltage is given by

$$V_{OUT} = 1.23V (1 + R1/R2)$$

Resistors R1 and R2 divide the output down so it can be compared with the LM1577-ADJ/LM2577-ADJ internal 1.23V reference. For a given desired output voltage  $V_{OUT}$ , select R1 and R2 so that

$$\frac{R1}{R2} = \frac{V_{OUT}}{1.23V} - 1$$

### 4. Input Capacitor Selection ( $C_{IN}$ )

The switching action in the step-up regulator causes a triangular ripple current to be drawn from the supply source. This in turn causes noise to appear on the supply voltage. For proper operation of the LM1577, the input voltage should be decoupled. Bypassing the Input Voltage pin directly to ground with a good quality, low ESR, 0.1  $\mu$ F capacitor (leads as short as possible) is normally sufficient.

**Cornell Dublier** — Types 239, 250, 251, UFT, 300, or 350

P.O. Box 128, Pickens, SC 29671  
(803) 878-6311

**Nichicon** — Types PF, PX, or PZ

927 East Parkway,  
Schaumburg, IL 60173  
(708) 843-7500

**Sprague** — Types 672D, 673D, or 674D

Box 1, Sprague Road,  
Lansing, NC 28643  
(919) 384-2551

**United Chemi-Con** — Types LX, SXF, or SXJ

9801 West Higgins Road,  
Rosemont, IL 60018  
(708) 696-2000

FIGURE 11. Aluminum Electrolytic Capacitors Recommended for Switching Regulators

If the LM1577 is located far from the supply source filter capacitors, an additional large electrolytic capacitor (e.g. 47  $\mu$ F) is often required.

### 5. Diode Selection (D)

The switching diode used in the boost regulator must withstand a reverse voltage equal to the circuit output voltage, and must conduct the peak output current of the LM2577. A suitable diode must have a minimum reverse breakdown voltage greater than the circuit output voltage, and should be rated for average and peak current greater than  $I_{LOAD(MAX)}$  and  $I_{D(PK)}$ . Schottky barrier diodes are often favored for use in switching regulators. Their low forward voltage drop allows higher regulator efficiency than if a (less expensive) fast recovery diode was used. See Figure 12 for recommended part numbers and voltage ratings of 1A and 3A diodes.

| $V_{OUT}$<br>(max) | Schottky                    |                             | Fast Recovery                       |                                   |
|--------------------|-----------------------------|-----------------------------|-------------------------------------|-----------------------------------|
|                    | 1A                          | 3A                          | 1A                                  | 3A                                |
| 20V                | 1N5817<br>MBR120P           | 1N5820<br>MBR320P           |                                     |                                   |
| 30V                | 1N5818<br>MBR130P<br>11DQ03 | 1N5821<br>MBR330P<br>31DQ03 |                                     |                                   |
| 40V                | 1N5819<br>MBR140P<br>11DQ04 | 1N5822<br>MBR340P<br>31DQ04 |                                     |                                   |
| 50V                | MBR150<br>11DQ05            | MBR350<br>31DQ05            | 1N4933<br>MUR105                    |                                   |
| 100V               |                             |                             | 1N4934<br>HER102<br>MUR110<br>10DL1 | MR851<br>30DL1<br>MR831<br>HER302 |

FIGURE 12. Diode Selection Chart

### BOOST REGULATOR CIRCUIT EXAMPLE

By adding a few external components (as shown in Figure 13), the LM2577 can be used to produce a regulated output voltage that is greater than the applied input voltage. Typical performance of this regulator is shown in Figure 14 and Figure 15. The switching waveforms observed during the operation of this circuit are shown in Figure 16.

# LM2575

## 1.0 A, Adjustable Output Voltage, Step-Down Switching Regulator

The LM2575 series of regulators are monolithic integrated circuits ideally suited for easy and convenient design of a step-down switching regulator (buck converter). All circuits of this series are capable of driving a 1.0 A load with excellent line and load regulation. These devices are available in fixed output voltages of 3.3 V, 5.0 V, 12 V, 15 V, and an adjustable output version.

These regulators were designed to minimize the number of external components to simplify the power supply design. Standard series of inductors optimized for use with the LM2575 are offered by several different inductor manufacturers.

Since the LM2575 converter is a switch-mode power supply, its efficiency is significantly higher in comparison with popular three-terminal linear regulators, especially with higher input voltages. In many cases, the power dissipated by the LM2575 regulator is so low, that no heatsink is required or its size could be reduced dramatically.

The LM2575 features include a guaranteed  $\pm 4\%$  tolerance on output voltage within specified input voltages and output load conditions, and  $\pm 10\%$  on the oscillator frequency ( $\pm 2\%$  over  $0^\circ\text{C}$  to  $125^\circ\text{C}$ ). External shutdown is included, featuring 80  $\mu\text{A}$  typical standby current. The output switch includes cycle-by-cycle current limiting, as well as thermal shutdown for full protection under fault conditions.



ON Semiconductor®

<http://onsemi.com>




TO-220  
TV SUFFIX  
CASE 314B

Heatsink surface connected to Pin 3



TO-220  
T SUFFIX  
CASE 314D

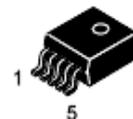
- Pin
1.  $V_{in}$
  2. Output
  3. Ground
  4. Feedback
  5. ON/OFF



D2PAK  
D2T SUFFIX  
CASE 936A

Heatsink surface (shown as terminal 6 in case outline drawing) is connected to Pin 3
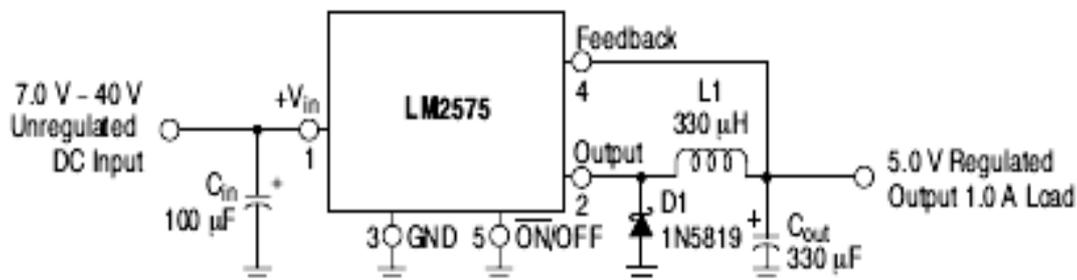
### Typical Application (Fixed Output Voltage Versions)



# LM2575

## PIN FUNCTION DESCRIPTION

| Pin | Symbol              | Description (Refer to Figure 1)   |
|-----|---------------------|---|
| 1   | $V_{in}$            | This pin is the positive input supply for the LM2575 step-down switching regulator. In order to minimize voltage transients and to supply the switching currents needed by the regulator, a suitable input bypass capacitor must be present ( $C_{in}$ in Figure 1).  |
| 2   | Output              | This is the emitter of the internal switch. The saturation voltage $V_{sat}$ of this output switch is typically 1.0 V. It should be kept in mind that the PCB area connected to this pin should be kept to a minimum in order to minimize coupling to sensitive circuitry.  |
| 3   | GND                 | Circuit ground pin. See the information about the printed circuit board layout.   |
| 4   | Feedback            | This pin senses regulated output voltage to complete the feedback loop. The signal is divided by the internal resistor divider network R2, R1 and applied to the non-inverting input of the internal error amplifier. In the Adjustable version of the LM2575 switching regulator this pin is the direct input of the error amplifier and the resistor network R2, R1 is connected externally to allow programming of the output voltage. |
| 5   | $\overline{ON/OFF}$ | It allows the switching regulator circuit to be shut down using logic level signals, thus dropping the total input supply current to approximately 80 $\mu$ A. The input threshold voltage is typically 1.4 V. Applying a voltage above this value (up to $+V_{in}$ ) shuts the regulator off. If the voltage applied to this pin is lower than 1.4 V or if this pin is connected to ground, the regulator will be in the "on" condition. |

## DESIGN PROCEDURE

### Buck Converter Basics

The LM2575 is a "Buck" or Step-Down Converter which is the most elementary forward-mode converter. Its basic schematic can be seen in Figure 15.

The operation of this regulator topology has two distinct time periods. The first one occurs when the series switch is on, the input voltage is connected to the input of the inductor.

The output of the inductor is the output voltage, and the rectifier (or catch diode) is reverse biased. During this period, since there is a constant voltage source connected across the inductor, the inductor current begins to linearly ramp upwards, as described by the following equation:

$$I_{L(on)} = \frac{(V_{in} - V_{out}) t_{on}}{L}$$

During this "on" period, energy is stored within the core material in the form of magnetic flux. If the inductor is properly designed, there is sufficient energy stored to carry the requirements of the load during the "off" period.

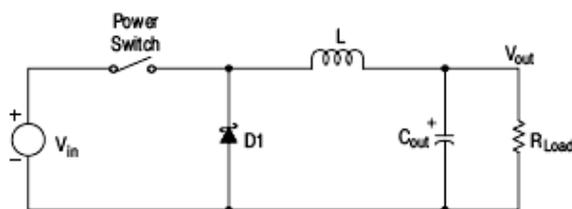


Figure 15. Basic Buck Converter

The next period is the "off" period of the power switch. When the power switch turns off, the voltage across the inductor reverses its polarity and is clamped at one diode voltage drop below ground by catch diode. Current now flows through the catch diode thus maintaining the load current loop. This removes the stored energy from the inductor.

The inductor current during this time is:

$$I_{L(off)} = \frac{(V_{out} - V_D) t_{off}}{L}$$

This period ends when the power switch is once again turned on. Regulation of the converter is accomplished by varying the duty cycle of the power switch. It is possible to describe the duty cycle as follows:

$$d = \frac{t_{on}}{T}, \text{ where } T \text{ is the period of switching.}$$

For the buck converter with ideal components, the duty cycle can also be described as:

$$d = \frac{V_{out}}{V_{in}}$$

Figure 16 shows the buck converter idealized waveforms of the catch diode voltage and the inductor current.

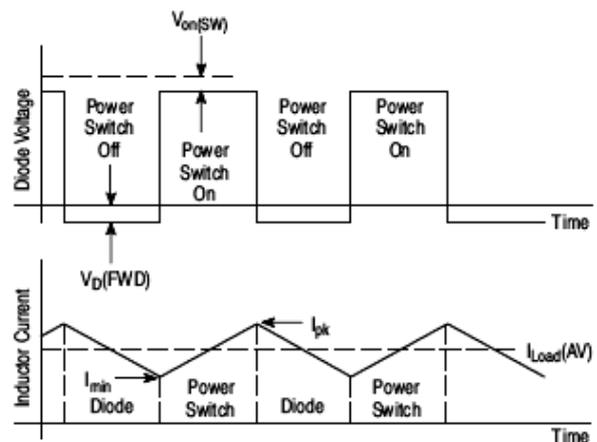


Figure 16. Buck Converter Idealized Waveforms

## LM2575

**Procedure (Fixed Output Voltage Version)** In order to simplify the switching regulator design, a step-by-step design procedure and example is provided.

| Procedure   | Example   |
|---|---|
| <p><b>Given Parameters:</b><br/> <math>V_{out}</math> = Regulated Output Voltage (3.3 V, 5.0 V, 12 V or 15 V)<br/> <math>V_{in(max)}</math> = Maximum DC Input Voltage<br/> <math>I_{Load(max)}</math> = Maximum Load Current</p>   | <p><b>Given Parameters:</b><br/> <math>V_{out}</math> = 5.0 V<br/> <math>V_{in(max)}</math> = 20 V<br/> <math>I_{Load(max)}</math> = 0.8 A</p>  |
| <p><b>1. Controller IC Selection</b><br/>           According to the required input voltage, output voltage and current, select the appropriate type of the controller IC output voltage version.</p>   | <p><b>1. Controller IC Selection</b><br/>           According to the required input voltage, output voltage, current polarity and current value, use the LM2575-5 controller IC</p>   |
| <p><b>2. Input Capacitor Selection (<math>C_{in}</math>)</b><br/>           To prevent large voltage transients from appearing at the input and for stable operation of the converter, an aluminium or tantalum electrolytic bypass capacitor is needed between the input pin +<math>V_{in}</math> and ground pin GND. This capacitor should be located close to the IC using short leads. This capacitor should have a low ESR (Equivalent Series Resistance) value.</p>   | <p><b>2. Input Capacitor Selection (<math>C_{in}</math>)</b><br/>           A 47 <math>\mu</math>F, 25 V aluminium electrolytic capacitor located near to the input and ground pins provides sufficient bypassing.</p>  |
| <p><b>3. Catch Diode Selection (D1)</b><br/>           A. Since the diode maximum peak current exceeds the regulator maximum load current the catch diode current rating must be at least 1.2 times greater than the maximum load current. For a robust design the diode should have a current rating equal to the maximum current limit of the LM2575 to be able to withstand a continuous output short<br/>           B. The reverse voltage rating of the diode should be at least 1.25 times the maximum input voltage.</p>   | <p><b>3. Catch Diode Selection (D1)</b><br/>           A. For this example the current rating of the diode is 1.0 A.<br/><br/>           B. Use a 30 V 1N5818 Schottky diode, or any of the suggested fast recovery diodes shown in the Table 4.</p>  |
| <p><b>4. Inductor Selection (L1)</b><br/>           A. According to the required working conditions, select the correct inductor value using the selection guide from Figures 17 to 21.<br/>           B. From the appropriate inductor selection guide, identify the inductance region intersected by the Maximum Input Voltage line and the Maximum Load Current line. Each region is identified by an inductance value and an inductor code.<br/>           C. Select an appropriate inductor from the several different manufacturers part numbers listed in Table 1 or Table 2. When using Table 2 for selecting the right inductor the designer must realize that the inductor current rating must be higher than the maximum peak current flowing through the inductor. This maximum peak current can be calculated as follows:<br/> <math display="block">I_{p(max)} = I_{Load(max)} + \frac{(V_{in} - V_{out}) t_{on}}{2L}</math>           where <math>t_{on}</math> is the "on" time of the power switch and<br/> <math display="block">t_{on} = \frac{V_{out}}{V_{in}} \times \frac{1}{f_{osc}}</math>           For additional information about the inductor, see the inductor section in the "External Components" section of this data sheet.</p> | <p><b>4. Inductor Selection (L1)</b><br/>           A. Use the inductor selection guide shown in Figures 17 to 21.<br/><br/>           B. From the selection guide, the inductance area intersected by the 20 V line and 0.8 A line is L330.<br/><br/>           C. Inductor value required is 330 <math>\mu</math>H. From the Table 1 or Table 2, choose an inductor from any of the listed manufacturers.</p> |

## LM2575

**Procedure (Fixed Output Voltage Version) (continued)** In order to simplify the switching regulator design, a step-by-step design procedure and example is provided.

| Procedure   | Example   |
|---|---|
| <p><b>5. Output Capacitor Selection (<math>C_{out}</math>)</b></p> <p>A. Since the LM2575 is a forward-mode switching regulator with voltage mode control, its open loop 2-pole-2-zero frequency characteristic has the dominant pole-pair determined by the output capacitor and inductor values. For stable operation and an acceptable ripple voltage, (approximately 1% of the output voltage) a value between 100 <math>\mu</math>F and 470 <math>\mu</math>F is recommended.</p> <p>B. Due to the fact that the higher voltage electrolytic capacitors generally have lower ESR (Equivalent Series Resistance) numbers, the output capacitor's voltage rating should be at least 1.5 times greater than the output voltage. For a 5.0 V regulator, a rating at least 8V is appropriate, and a 10 V or 16 V rating is recommended.</p> | <p><b>5. Output Capacitor Selection (<math>C_{out}</math>)</b></p> <p>A. <math>C_{out}</math> = 100 <math>\mu</math>F to 470 <math>\mu</math>F standard aluminium electrolytic.</p><br><p>B. Capacitor voltage rating = 16 V.</p> |

### Procedure (Adjustable Output Version: LM2575-Adj)

| Procedure  | Example  |
|--|--|
| <p><b>Given Parameters:</b><br/> <math>V_{out}</math> = Regulated Output Voltage<br/> <math>V_{in(max)}</math> = Maximum DC Input Voltage<br/> <math>I_{Load(max)}</math> = Maximum Load Current</p>   | <p><b>Given Parameters:</b><br/> <math>V_{out}</math> = 8.0 V<br/> <math>V_{in(max)}</math> = 12 V<br/> <math>I_{Load(max)}</math> = 1.0 A</p>   |
| <p><b>1. Programming Output Voltage</b><br/>           To select the right programming resistor R1 and R2 value (see Figure 14) use the following formula:</p> $V_{out} = V_{ref} \left( 1 + \frac{R2}{R1} \right) \text{ where } V_{ref} = 1.23 \text{ V}$ <p>Resistor R1 can be between 1.0 k and 5.0 k<math>\Omega</math>. (For best temperature coefficient and stability with time, use 1% metal film resistors).</p> $R2 = R1 \left( \frac{V_{out}}{V_{ref}} - 1 \right)$  | <p><b>1. Programming Output Voltage (selecting R1 and R2)</b><br/>           Select R1 and R2:</p> $V_{out} = 1.23 \left( 1 + \frac{R2}{R1} \right) \text{ Select } R1 = 1.8 \text{ k}\Omega$ $R2 = R1 \left( \frac{V_{out}}{V_{ref}} - 1 \right) = 1.8 \text{ k} \left( \frac{8.0 \text{ V}}{1.23 \text{ V}} - 1 \right)$ <p>R2 = 9.91 k<math>\Omega</math>, choose a 9.88 k metal film resistor.</p> |
| <p><b>2. Input Capacitor Selection (<math>C_{in}</math>)</b><br/>           To prevent large voltage transients from appearing at the input and for stable operation of the converter, an aluminium or tantalum electrolytic bypass capacitor is needed between the input pin +<math>V_{in}</math> and ground pin GND. This capacitor should be located close to the IC using short leads. This capacitor should have a low ESR (Equivalent Series Resistance) value.</p> <p>For additional information see input capacitor section in the "External Components" section of this data sheet.</p> | <p><b>2. Input Capacitor Selection (<math>C_{in}</math>)</b><br/>           A 100 <math>\mu</math>F aluminium electrolytic capacitor located near the input and ground pin provides sufficient bypassing.</p>  |
| <p><b>3. Catch Diode Selection (D1)</b></p> <p>A. Since the diode maximum peak current exceeds the regulator maximum load current the catch diode current rating must be at least 1.2 times greater than the maximum load current. For a robust design, the diode should have a current rating equal to the maximum current limit of the LM2575 to be able to withstand a continuous output short.</p> <p>B. The reverse voltage rating of the diode should be at least 1.25 times the maximum input voltage.</p>  | <p><b>3. Catch Diode Selection (D1)</b></p> <p>A. For this example, a 3.0 A current rating is adequate.</p><br><p>B. Use a 20 V 1N5820 or MBR320 Schottky diode or any suggested fast recovery diode in the Table 4.</p>   |

## LM2575

### Procedure (Adjustable Output Version: LM2575-Adj) (continued)

| Procedure  | Example   |
|--|---|
| <p><b>4. Inductor Selection (L1)</b></p> <p>A. Use the following formula to calculate the inductor Volt x microsecond [V x <math>\mu</math>s] constant:</p> $E \times T = (V_{in} - V_{out}) \frac{V_{out}}{V_{on}} \times \frac{10^6}{F[\text{Hz}]} \text{ [V x } \mu\text{s]}$ <p>B. Match the calculated E x T value with the corresponding number on the vertical axis of the Inductor Value Selection Guide shown in Figure 21. This E x T constant is a measure of the energy handling capability of an inductor and is dependent upon the type of core, the core area, the number of turns, and the duty cycle.</p> <p>C. Next step is to identify the inductance region intersected by the E x T value and the maximum load current value on the horizontal axis shown in Figure 21.</p> <p>D. From the inductor code, identify the inductor value. Then select an appropriate inductor from the Table 1 or Table 2. The inductor chosen must be rated for a switching frequency of 52 kHz and for a current rating of <math>1.15 \times I_{load}</math>. The inductor current rating can also be determined by calculating the inductor peak current:</p> $I_{p(\text{max})} = I_{\text{Load}(\text{max})} + \frac{(V_{in} - V_{out}) t_{on}}{2L}$ <p>where <math>t_{on}</math> is the "on" time of the power switch and</p> $t_{on} = \frac{V_{out}}{V_{in}} \times \frac{1}{f_{osc}}$ <p>For additional information about the inductor, see the inductor section in the "External Components" section of this data sheet.</p> | <p><b>4. Inductor Selection (L1)</b></p> <p>A. Calculate E x T [V x <math>\mu</math>s] constant:</p> $E \times T = (12 - 8.0) \times \frac{8.0}{12} \times \frac{1000}{52} = 51 \text{ [V x } \mu\text{s]}$ <p>B. E x T = 51 [V x <math>\mu</math>s]</p> <p>C. <math>I_{\text{Load}(\text{max})} = 1.0 \text{ A}</math><br/>Inductance Region = L220</p> <p>D. Proper inductor value = 220 <math>\mu</math>H<br/>Choose the inductor from the Table 1 or Table 2.</p> |
| <p><b>5. Output Capacitor Selection (<math>C_{out}</math>)</b></p> <p>A. Since the LM2575 is a forward-mode switching regulator with voltage mode control, its open loop 2-pole-2-zero frequency characteristic has the dominant pole-pair determined by the output capacitor and inductor values.</p> <p>For stable operation, the capacitor must satisfy the following requirement:</p> $C_{out} \geq 7.785 \frac{V_{in(\text{max})}}{V_{out} \times L [\mu\text{H}]} \text{ [}\mu\text{F]}$ <p>B. Capacitor values between 10 <math>\mu</math>F and 2000 <math>\mu</math>F will satisfy the loop requirements for stable operation. To achieve an acceptable output ripple voltage and transient response, the output capacitor may need to be several times larger than the above formula yields.</p> <p>C. Due to the fact that the higher voltage electrolytic capacitors generally have lower ESR (Equivalent Series Resistance) numbers, the output capacitor's voltage rating should be at least 1.5 times greater than the output voltage. For a 5.0 V regulator, a rating of at least 8V is appropriate, and a 10 V or 16 V rating is recommended.</p>  | <p><b>5. Output Capacitor Selection (<math>C_{out}</math>)</b></p> <p>A.</p> $C_{out} \geq 7.785 \frac{12}{8.220} = 53 \mu\text{F}$ <p>To achieve an acceptable ripple voltage, select <math>C_{out} = 100 \mu\text{F}</math> electrolytic capacitor.</p>   |

# LM2575

## INDUCTOR VALUE SELECTION GUIDE

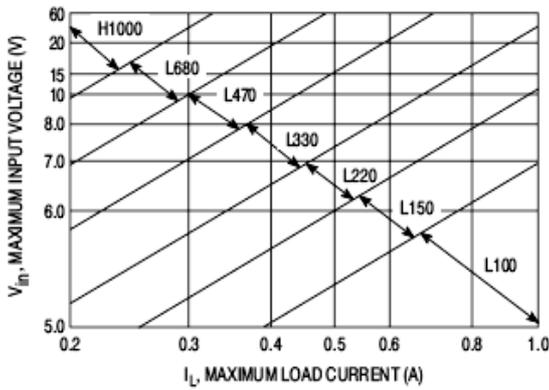


Figure 17. LM2575-3.3

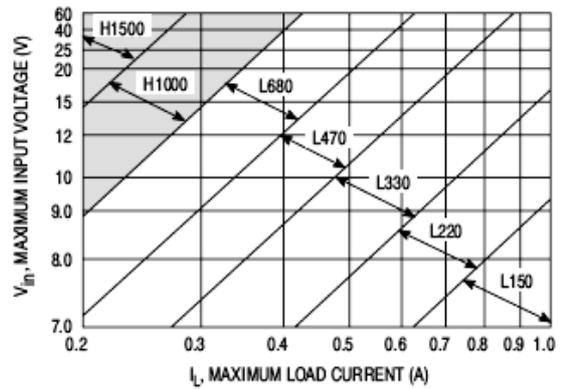


Figure 18. LM2575-5.0

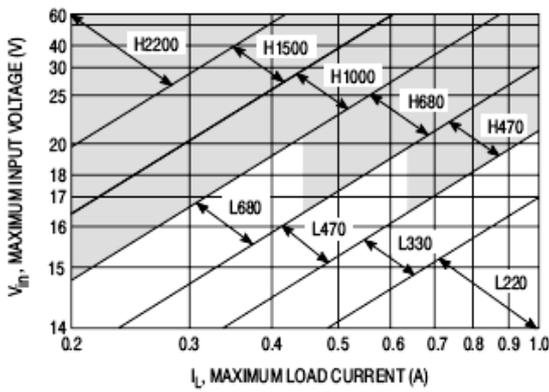


Figure 19. LM2575-12

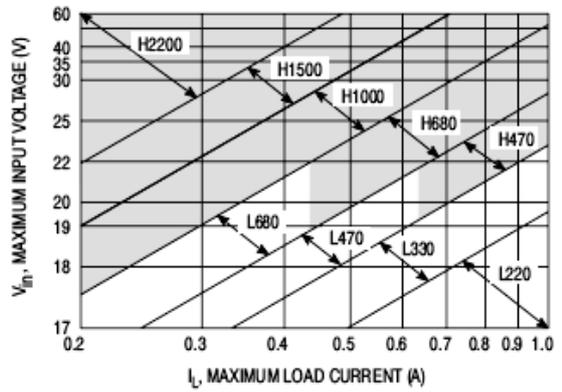


Figure 20. LM2575-15

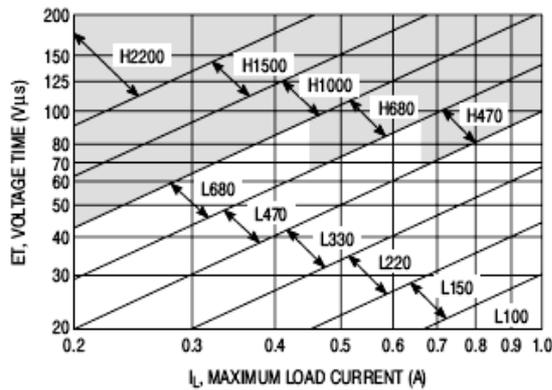


Figure 21. LM2575-Adj

NOTE: This Inductor Value Selection Guide is applicable for continuous mode only.

## LM2575

**Table 1. Inductor Selection Guide**

| Inductor Code | Inductor Value | Pulse Eng | Renco  | AIE      | Tech 39   |
|---------------|----------------|-----------|--------|----------|-----------|
| L100          | 100 $\mu$ H    | PE-92108  | RL2444 | 415-0930 | 77 308 BV |
| L150          | 150 $\mu$ H    | PE-53113  | RL1954 | 415-0953 | 77 358 BV |
| L220          | 220 $\mu$ H    | PE-52626  | RL1953 | 415-0922 | 77 408 BV |
| L330          | 330 $\mu$ H    | PE-52627  | RL1952 | 415-0926 | 77 458 BV |
| L470          | 470 $\mu$ H    | PE-53114  | RL1951 | 415-0927 | -         |
| L680          | 680 $\mu$ H    | PE-52629  | RL1950 | 415-0928 | 77 508 BV |
| H150          | 150 $\mu$ H    | PE-53115  | RL2445 | 415-0936 | 77 368 BV |
| H220          | 220 $\mu$ H    | PE-53116  | RL2446 | 430-0636 | 77 410 BV |
| H330          | 330 $\mu$ H    | PE-53117  | RL2447 | 430-0635 | 77 460 BV |
| H470          | 470 $\mu$ H    | PE-53118  | RL1961 | 430-0634 | -         |
| H680          | 680 $\mu$ H    | PE-53119  | RL1960 | 415-0935 | 77 510 BV |
| H1000         | 1000 $\mu$ H   | PE-53120  | RL1959 | 415-0934 | 77 558 BV |
| H1500         | 1500 $\mu$ H   | PE-53121  | RL1958 | 415-0933 | -         |
| H2200         | 2200 $\mu$ H   | PE-53122  | RL2448 | 415-0945 | 77 610 BV |

**Table 2. Inductor Selection Guide**


| Inductance<br>( $\mu$ H) | Current<br>(A) | Schott   |          | Renco         |            | Pulse Engineering |            | Coilcraft   |
|--------------------------|----------------|----------|----------|---------------|------------|-------------------|------------|-------------|
|                          |                | THT      | SMT      | THT           | SMT        | THT               | SMT        | SMT         |
| 68                       | 0.32           | 67143940 | 67144310 | RL-1284-68-43 | RL1500-68  | PE-53804          | PE-53804-S | DO1608-68   |
|                          | 0.58           | 67143990 | 67144360 | RL-5470-6     | RL1500-68  | PE-53812          | PE-53812-S | DO3308-683  |
|                          | 0.99           | 67144070 | 67144450 | RL-5471-5     | RL1500-68  | PE-53821          | PE-53821-S | DO3316-683  |
|                          | 1.78           | 67144140 | 67144520 | RL-5471-5     | -          | PE-53830          | PE-53830-S | DO5022P-683 |
| 100                      | 0.48           | 67143980 | 67144350 | RL-5470-5     | RL1500-100 | PE-53811          | PE-53811-S | DO3308-104  |
|                          | 0.82           | 67144060 | 67144440 | RL-5471-4     | RL1500-100 | PE-53820          | PE-53820-S | DO3316-104  |
|                          | 1.47           | 67144130 | 67144510 | RL-5471-4     | -          | PE-53829          | PE-53829-S | DO5022P-104 |
| 150                      | 0.39           | -        | 67144340 | RL-5470-4     | RL1500-150 | PE-53810          | PE-53810-S | DO3308-154  |
|                          | 0.66           | 67144050 | 67144430 | RL-5471-3     | RL1500-150 | PE-53819          | PE-53819-S | DO3316-154  |
|                          | 1.20           | 67144120 | 67144500 | RL-5471-3     | -          | PE-53828          | PE-53828-S | DO5022P-154 |
| 220                      | 0.32           | 67143960 | 67144330 | RL-5470-3     | RL1500-220 | PE-53809          | PE-53809-S | DO3308-224  |
|                          | 0.55           | 67144040 | 67144420 | RL-5471-2     | RL1500-220 | PE-53818          | PE-53818-S | DO3316-224  |
|                          | 1.00           | 67144110 | 67144490 | RL-5471-2     | -          | PE-53827          | PE-53827-S | DO5022P-224 |
| 330                      | 0.42           | 67144030 | 67144410 | RL-5471-1     | RL1500-330 | PE-53817          | PE-53817-S | DO3316-334  |
|                          | 0.80           | 67144100 | 67144480 | RL-5471-1     | -          | PE-53826          | PE-53826-S | DO5022P-334 |

NOTE: Table 1 and Table 2 of this Indicator Selection Guide shows some examples of different manufacturer products suitable for design with the LM2575.

# Annexe 5 : Diode 1N5822


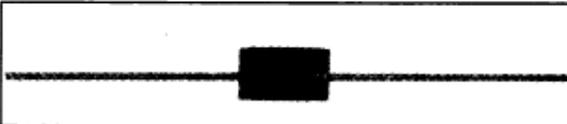
## 1N5820 THRU 1N5822 3.0 AMPS. SCHOTTKY BARRIER RECTIFIERS



**FEATURES**

- \* Low forward voltage drop
- \* High current capability
- \* High reliability
- \* High surge current capability


**MECHANICAL DATA**

- \* Case: DO-201 AD Molded plastic
- \* Epoxy: UL 94V - 0 rate flame retardant
- \* Lead: Axial leads, solderable per MIL - STD - 202, method 208 guaranteed
- \* Polarity: Color band denotes cathode end
- \* Weight: 1.10grams

**VOLTAGE RANGE**  
20 to 40 volts

**CURRENT**  
3.0 Amperes

**DO-201AD**

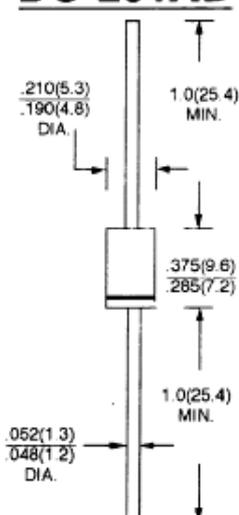

Dimensions in inches and (millimeters)

### MAXIMUM RATINGS AND ELECTRICAL CHARACTERISTICS

Rating at 25°C ambient temperature unless otherwise specified.  
Single phase, half wave, 60 Hz, resistive or inductive load.  
For capacitive load, derate current by 20%

| TYPE NUMBER   | SYMBOLS         | 1N5820      | 1N5821 | 1N5822 | UNITS        |
|---|-----------------|-------------|--------|--------|--------------|
| Maximum Recurrent Peak Reverse Voltage  | $V_{RRM}$       | 20          | 30     | 40     | V            |
| Maximum RMS Voltage   | $V_{RMS}$       | 14          | 21     | 28     | V            |
| Maximum DC Blocking Voltage   | $V_{DC}$        | 20          | 30     | 40     | V            |
| Maximum Average Forward Rectified Current @ $T_L = 90^\circ C$  | $I_{F(AV)}$     | 3.0         |        |        | A            |
| Peak Forward Surge Current (8.3 ms half sine)   | $I_{FSM}$       | 80          |        |        | A            |
| Maximum Instantaneous Forward Voltage @ 3.0A (Note 1)   | $V_F$           | 0.475       | 0.500  | 0.525  | V            |
| Maximum Instantaneous Forward Voltage @ 9.0A  | $V_{FM}$        | 0.850       | 0.900  | 0.950  | V            |
| Maximum D. C Reverse Current at Rated D. C Blocking Voltage @ $T_A = 25^\circ C$<br>@ $T_A = 100^\circ C$ | $I_R$           | 2.0<br>20   |        |        | mA           |
| Typical Thermal Resistance (Note 2)   | $R_{\theta JA}$ | 40          |        |        | $^\circ C/W$ |
| Typical Junction Capacitance (Note 3)   | $C_J$           | 300         |        |        | pF           |
| Operating and Storage Temperature Range   | $T_J$           | -65 to +125 |        |        | $^\circ C$   |

**NOTE:** (1) Pulse test: 300µs pulse width, 1% duty cycle  
(2) Thermal Resistance Junction to Ambient Vertical PC Board Mounted, .0500" (12.7mm) Lead Length with 2.5 x 2.5" (63.5 x 63.5mm) copper pads.  
(3) Measured at 1 MHz and applied reverse voltage of 4.0V D. C.

# Annexe 6 : Diode MBR 2045CT

## MBR2045CT

### SWITCHMODE™ Power Rectifier

#### Features and Benefits

- Low Forward Voltage
- Low Power Loss / High Efficiency
- High Surge Capacity
- 175°C Operating Junction Temperature
- 20 A Total (10 A Per Diode Leg)
- Pb-Free Package is Available\*

#### Applications

- Power Supply – Output Rectification
- Power Management
- Instrumentation

#### Mechanical Characteristics


- Case: Epoxy, Molded
- Epoxy Meets UL 94, V-0 @ 0.125 in
- Weight: 1.9 Grams (Approximately)
- Finish: All External Surfaces Corrosion Resistant and Terminal Leads are Readily Solderable
- Lead Temperature for Soldering Purposes: 260°C Max. for 10 Seconds
- ESD Rating: Human Body Model = 3B  
Machine Model = C



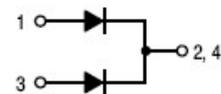
**ON Semiconductor®**

<http://onsemi.com>

**SCHOTTKY BARRIER  
RECTIFIER  
20 AMPERES, 45 VOLTS**



#### MARKING DIAGRAM

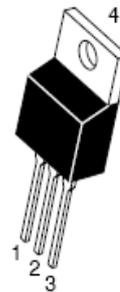

**TO-220AB  
CASE 221A  
STYLE 6**




A = Assembly Location  
Y = Year  
WW = Work Week  
MBR2045CT = Device Code  
G = Pb-Free Package  
AKA = Diode Polarity

#### ORDERING INFORMATION

| Device     | Package             | Shipping        |
|------------|---------------------|-----------------|
| MBR2045CT  | TO-220              | 50 Units / Rail |
| MBR2045CTG | TO-220<br>(Pb-Free) | 50 Units / Rail |

# Annexe 6 : Implantation des composants

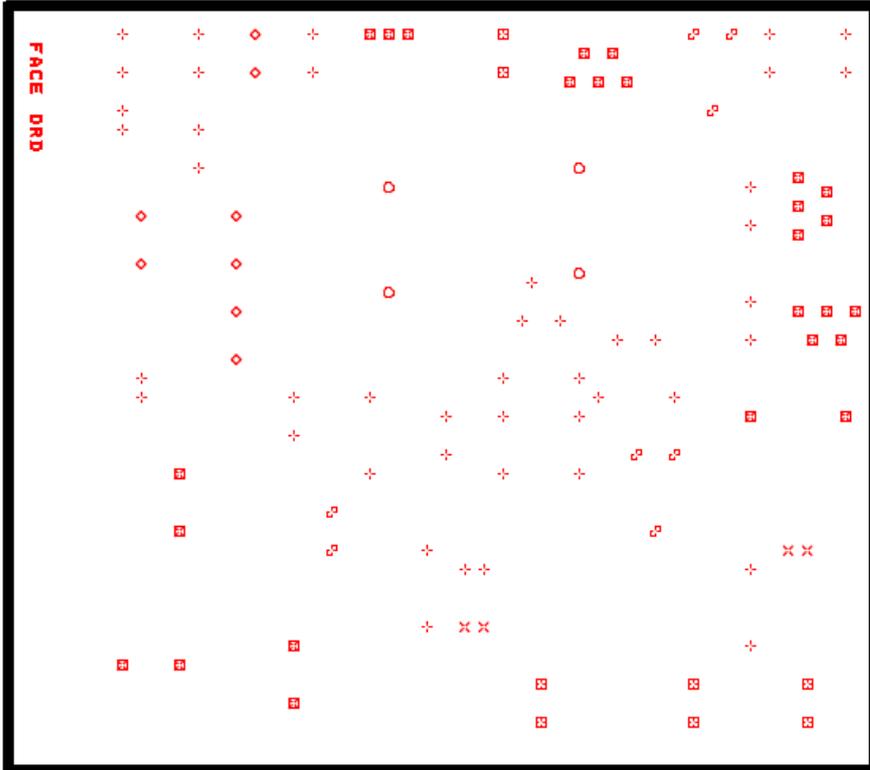

| DRILL CHART |          |     |     |      |
|-------------|----------|-----|-----|------|
| SYM         | DIAM     | TOL | QTY | NOTE |
| x           | 0.762 mm |     | 4   |      |
| +           | 0.787 mm |     | 45  |      |
| ◇           | 0.889 mm |     | 8   |      |
| ⊠           | 0.991 mm |     | 26  |      |
| ⊞           | 1.000 mm |     | 8   |      |
| ⊚           | 1.194 mm |     | 8   |      |
| ○           | 1.499 mm |     | 4   |      |
| TOTAL       |          |     | 103 |      |

Figure 8: Plan de perçage

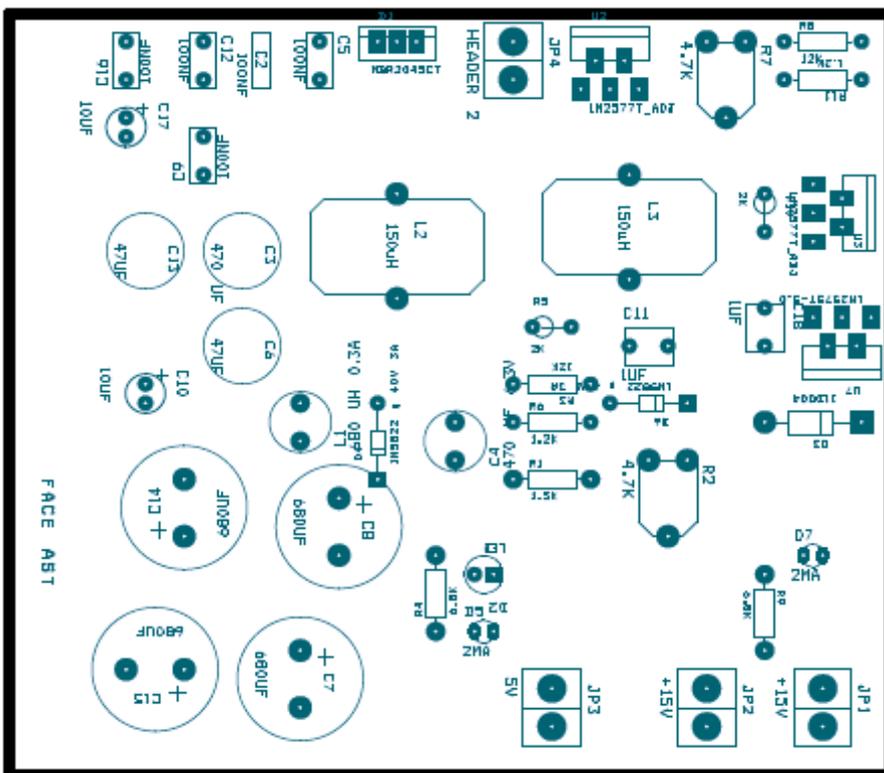


Figure 9: Emplacement des composants

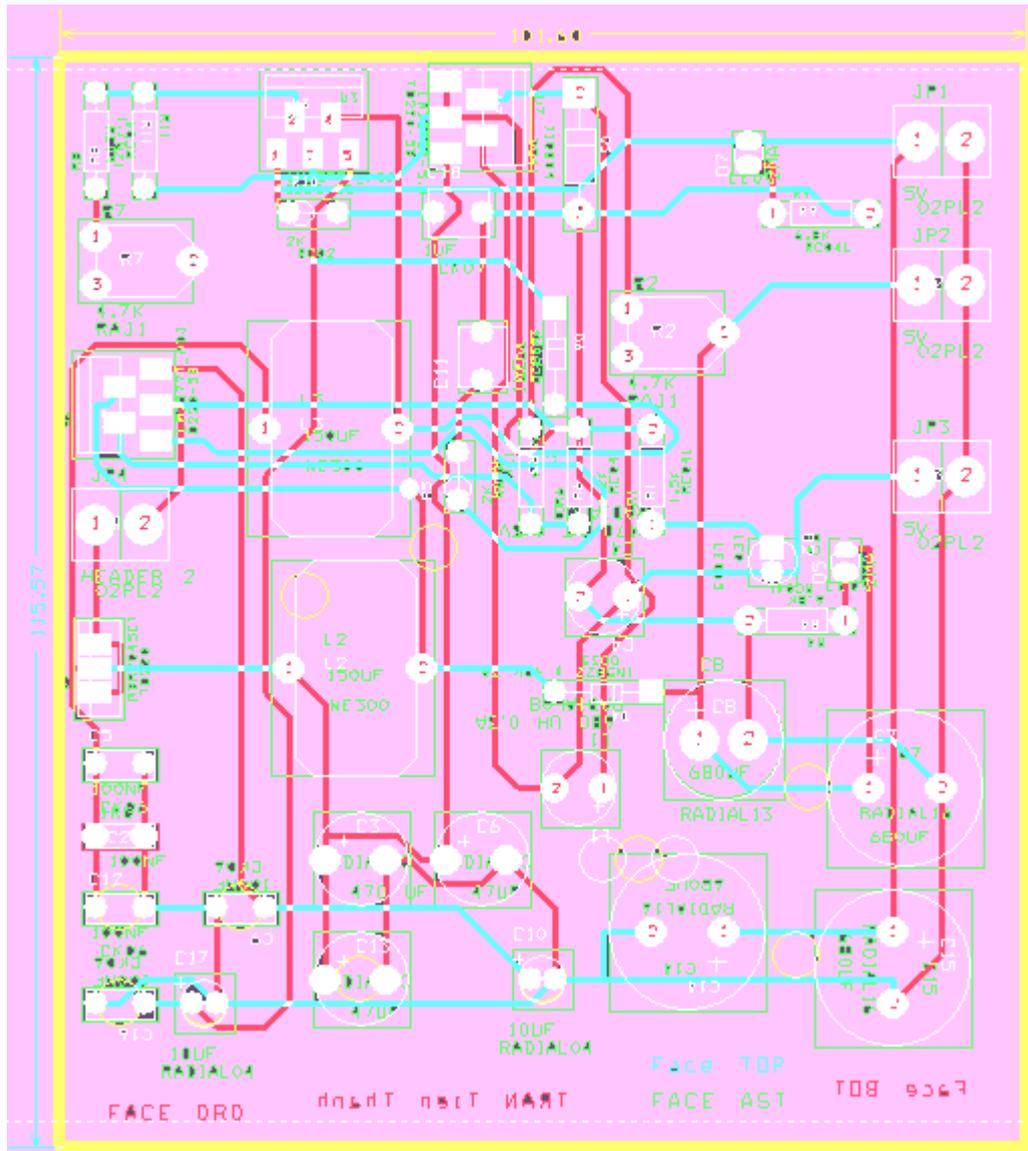


Figure 10: Typon complet

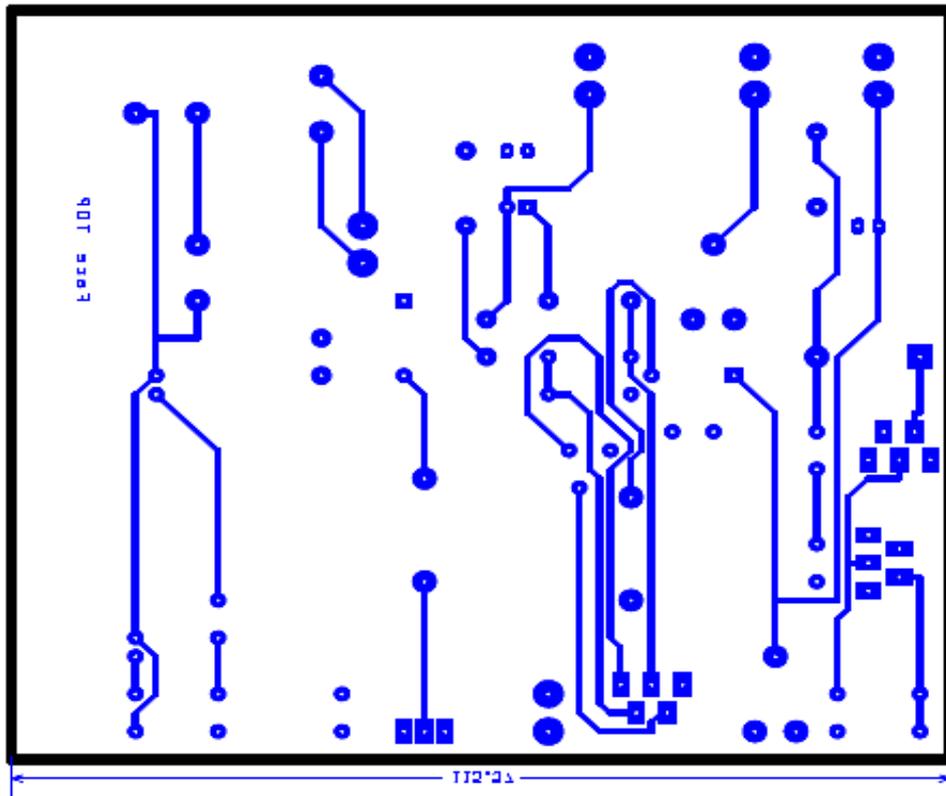


Figure 11 : Typon de la face de dessus(TOP)

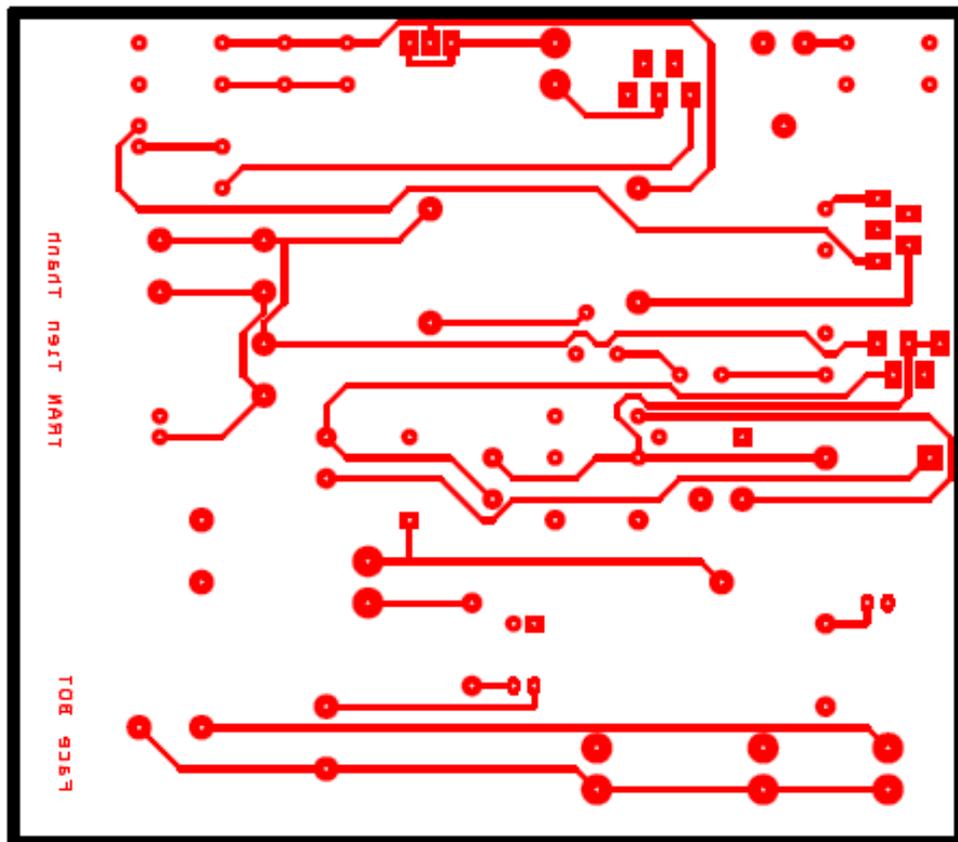


Figure 12 : Typon de la face de-dessous (BOTTOM)

# Bibliographie

## Sites internet utilisés :

<http://www.thierry-lequeu.fr/data/DATA347.HTM>

MBR2045CT :

<http://www.onsemi.com/pub/Collateral/MBR2045CT-D.PDF>

LM2575 :

<http://www.onsemi.com/pub/Collateral/LM2575-D.PDF>

LM2577T-ADJ :

<http://www.futurlec.com/Linear/LM2577T-ADJ.shtml>